

Major EEL 201 Digital Electronic Circuits

Time: 2 Hour

1/12/06


Max. Marks: 55

Name:	Entry #	Group #
-------	---------	---------

N.B.: Attempt all questions. Answer at the appropriate locations as indicated. For all calculations and rough work use the *reverse side / extra sheets* provided.

 Q1a. The 'resistor logic' circuit has binary inputs (A, B, C), of '0' V and '4' V (for 'low' and 'high' levels).

For $R = 2\text{ K}\Omega$, compute and fill the truth-table showing actual voltages for 'f' by filling in the given table on the right.




A	B	C	f volt
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	



Q1b. In the given NMOS transistors based logic circuit, T1 and T2 are placed in parallel. Supply voltages V_{DD} and V_{GG} are positive (set to Logic HIGH or 1). Write the truth-table for V_0 as a function of V_1 and V_2 .

(4 + 4 = 8 marks)

V_1	V_2	V_0

 

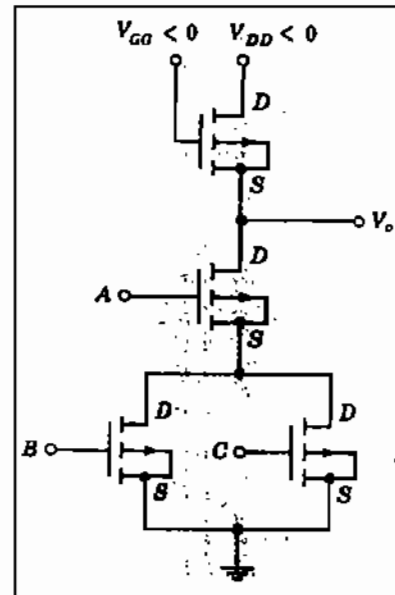 
Q2a. In the given PMOS transistor based logic circuit, output V_o is a function of three inputs A , B and C . A (OR, AND) logic gate circuit is also shown, but without proper inputs marked. For the two circuits to be equivalent, write the three inputs in the appropriate form, on the gate circuit. (3 marks)




Q2b. For the given CMOS circuit, write the output (OUT) as a function of the inputs (A, B, C, D) in SOP form. (5 marks)

Answer:

OUT =

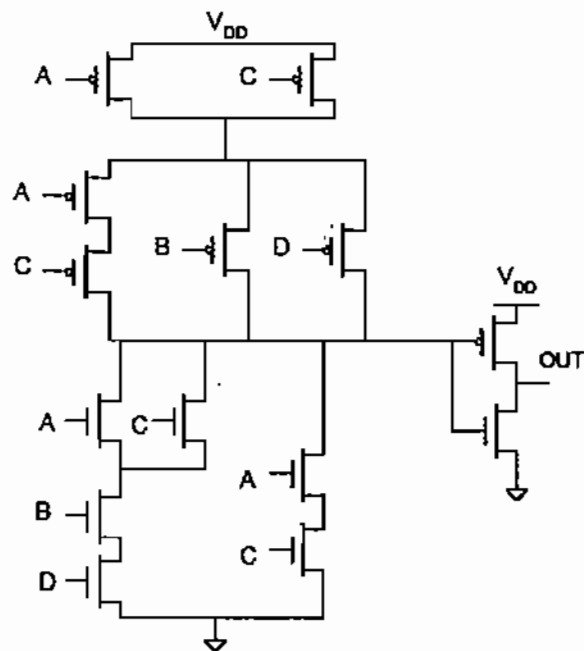

 Q3:- Using **diagram given below** compute 'Y' as a function of input signals. Using Boolean Difference method find out which of the **faults at 'h'** can not be tested? (Answer within 20 words to justify your **logic/proof** after derivations) Then compute all tests for the fault 'f's-a-0 by means of Boolean Difference method. (8)




Calculations: Y =

Answer: The fault/faults which can not be tested at 'h' is/are =
 The reason is...

The tests for 'f's-a-0 are as given below:

- a** **b** **c** **d**
 ↓ ↓ ↓ ↓
- 1st -----
- 2nd -----
- 3rd -----
- 4th -----

 Q4 (a):- Minimize the finite state machine given below using implication chart method.




B					
C					
D					
E					
F					
	A	B	C	D	E

Answer: The equivalent states are as ---

The minimized finite state machine is as:

 (b):- Convert the given Mealy machine into Moore machine.



ANSWER:- Draw equivalent machine below:

(6 + 3)

Q 5 (a):- Initial value of CY flag is 0. Write the value of CY flag and accumulator after the execution of instructions labeled as 1, 2, 3, 4, 5 and 6. Assume the value of mn H = 59 H

- MVI A, mn H
RAL
- (1) ADI E1 H
MVI B, 04 H
ANI FF H
- (2) ADC B
XRI mn H
MVI C, 01 H
- (3) RRC
MVI B, 10 H
- (4) ORA B
LXI H, 1234 H
LXI B, 5678 H
LXI D, 2468 H
ADD C
- (5) DAA
- (6) DAD B

Answers: List the answers as indicated

	CY	A = B₇	B₆	B₅	B₄	B₃	B₂	B₁	B₀
	↓	↓		↓	↓	↓	↓	↓	↓
1st	-----								
2nd	-----								
3rd	-----								
4th	-----								
5th	-----								
6th	-----								

(b) Find and write **only** accumulator values after the execution of instructions labeled as 1 and 2. (6+3)

```
                LXI B, 3386 H
                LXI D, 9533 H
                MVI A, 57 H
(1)            ADD C
                DAA
                CMP E
                SUB D
(2)            STC
```

Answer:

	A = B₇	B₆	B₅	B₄	B₃	B₂	B₁	B₀
	↓	↓	↓	↓	↓	↓	↓	↓
1st	-----							
2nd	-----							

Q6:- For the circuit given in figure (3) below answer the questions as indicated.

(6)

 


Figure 3

Here 3M3 implies 3.3 M. Ohm and similarly others.

(a) - What is the d.c. gain of the input stages (excluding the rightmost opamp)?

Answer:

(b) - If $C_1 = 1$ microfarad what is the lower cutoff frequency?

Answer:

(c) - If $C_2 = 0.0033$ microfarad what is the upper cutoff frequency?

Answer:

(d) - What is the overall gain of the circuit at the mid-band frequency?

Answer:

Q7:- Data appearing on a line synchronized with a clock should never have three or more consecutive 0's or four or more consecutive 1's.

Design a sequential circuit that will detect such sequences and generate an output of 1 whenever they occur. Construct appropriate timing diagrams for different combination of inputs. (7)

Answer:-