

## CRL712- RF and Microwave Active Circuits

Major Examination (Time: 3hr)  
Solve all questions.

09-05-2021

Maximum Marks-65

- Q1.** Two GaAs MESFET amplifiers with S-parameters listed below are used in a balanced amplifier configuration:
- Draw schematic of the balanced amplifier using branch line couplers.
  - Calculate the reflection coefficients and VSWRs at the input and output ports of the balanced amplifier.
  - Calculate overall power gain of the amplifier in dB.
- (4,4,2 marks)**

A			B		
Parameter	Mag.	Angle	Parameter	Mag.	Angle
$S_{11}$	0.75	$40^\circ$	$S_{11}$	0.82	$30^\circ$
$S_{12}$	0.15	$-30^\circ$	$S_{12}$	0.17	$-32^\circ$
$S_{21}$	7	$180^\circ$	$S_{21}$	7.5	$170^\circ$
$S_{22}$	0.6	$20^\circ$	$S_{22}$	0.75	$40^\circ$

- Q2.** A GaAs FET has the following scattering and noise parameters at 8 GHz  $S_{11} = 0.68 \angle -110^\circ$ ,  $S_{21} = 3.4 \angle 60^\circ$ ,  $S_{12} = 0.00$ ,  $S_{22} = 0.82 \angle -70^\circ$  ( $Z_0 = 50$  ohms):  $F_{\min} = 2.5$  dB,  $\Gamma_{\text{opt}} = 0.70 \angle 120^\circ$ ,  $R_N = 15$  ohms. Calculate source and load reflection coefficients for obtaining noise figure = 3 dB with maximum associated gain. Assume  $Z_0 = 50$  ohms.

$$N = \frac{F - F_{\min}}{4R_N / Z_0} |1 + \Gamma_{\text{opt}}|^2 \quad C_F = \frac{\Gamma_{\text{opt}}}{N + 1} \quad R_F = \frac{\sqrt{N(N + 1 - |\Gamma_{\text{opt}}|^2)}}{N + 1}$$

$$g_s = \frac{G_S}{G_{S_{\max}}} \quad C_S = \frac{g_s S_{11}^*}{1 - (1 - g_s) |S_{11}|^2} \text{ (Centre)} \quad R_S = \frac{\sqrt{1 - g_s} (1 - |S_{11}|^2)}{1 - (1 - g_s) |S_{11}|^2} \text{ (Radius)}$$

**(7,8 marks)**

- Q3.** The scattering parameters of an FET device at 10 GHz for different bias conditions are given below:

$$\begin{aligned} I_{ds}/I_{dss} \% = 20; & \quad S_{11} = 0.53 \angle -60^\circ, S_{12} = 0, S_{21} = 4.3 \angle 28^\circ, S_{22} = 0.75 \angle -150^\circ \\ I_{ds}/I_{dss} \% = 50; & \quad S_{11} = 0.54 \angle -50^\circ, S_{12} = 0, S_{21} = 4.8 \angle 29^\circ, S_{22} = 0.78 \angle -155^\circ \\ I_{ds}/I_{dss} \% = 100; & \quad S_{11} = 0.50 \angle -45^\circ, S_{12} = 0, S_{21} = 5.0 \angle 30^\circ, S_{22} = 0.8 \angle -160^\circ \end{aligned}$$

We want to design an amplifier using this FET device to achieve maximum gain. The source and load impedances are both  $50 \Omega$ .

- Determine if the maximum gain amplifier designed using the FET device will be stable.
- What is maximum gain obtained from the device in dB?
- Determine source match ( $\Gamma_s$ ) and load match ( $\Gamma_\ell$ ) required for achieving maximum gain.
- Determine maximum gain contribution in dB from the input matching and output matching networks.
- What is the maximum gain possible using the above FET in dB?
- Design the input matching network using a piece of 50-ohm transmission line and a quarter wave transformer.
- Design the output matching network using a piece of 50-ohm transmission line and short circuit 50-ohm stub.

(Marks 2,2,3,3,2,4,4)

**Q4.** Show how resistive loading can stabilize a device whose S-parameters at  $f = 750$  MHz:

$$S_{11} = 0.69 \angle 78^\circ, S_{12} = 0.033 \angle 41.4^\circ, S_{21} = 5.67 \angle 123^\circ, S_{22} = 0.84 \angle 25^\circ$$

$$K = \frac{1 + |S_{11}S_{22} - S_{12}S_{21}|^2 - |S_{11}|^2 - |S_{22}|^2}{2|S_{12}S_{21}|}; \Delta = S_{11}S_{22} - S_{21}S_{12}$$

$$C_L = \frac{(S_{22} - \Delta S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2} \text{ (Centre); } R_L = \left| \frac{S_{12}S_{21}}{|S_{22}|^2 - |\Delta|^2} \right| \text{ (Radius)}$$

$$C_S = \frac{(S_{11} - \Delta S_{22}^*)^*}{|S_{11}|^2 - |\Delta|^2} \text{ (Centre); } R_S = \left| \frac{S_{12}S_{21}}{|S_{11}|^2 - |\Delta|^2} \right| \text{ (Radius)}$$

Consider only two schemes of series resistive loading at the input and shunt resistive loading at the output of the device. Use Smith chart.

(Marks 5,5)

**Q5.** Two satellite receiver systems (a) and (b) have the following specifications for their components:

RF Amplifier:  $F=5$ dB,  $G=10$ dB

Mixer:  $L_c=5$ dB

IF Amplifier:  $F=2$ dB,  $G=15$ dB

Band Pass Filter:  $IL=2$ dB

Compare the two systems in terms of the overall gain and noise figure values.

(Marks 5,5)

