

CRL 712 RF and Microwave Active Circuits

Minor Exam-I (Time 2.00 hrs)

15th March 2021

Note: Solve all questions

Max Marks: 30

Q1. With the help of a neat diagram, explain the working principle of a non-reciprocal ferrite phase shifter.

[Marks 5]


Q2. A p-i-n diode chip is mounted across a 50-ohm microstrip line in shunt configuration. The frequency is 10 GHz, and the diode parameters are: $C_j=0.1\text{pF}$, $R_f=0.9\text{ ohms}$, $R_r=2.2\text{ ohms}$, $L_p=C_p=0$. Find the value of inductance placed across the diode to minimize the insertion loss for the ON-state of the switch. Calculate the resulting isolation and the insertion loss of the switch.

[Marks 4,2,2]

Q3. Consider a SPDT switch with identical p-i-n diodes shown below. The forward and reverse bias impedances of the diode are, $Z_f = 0.6\Omega$ and $Z_r = -j500\Omega$, respectively. The characteristic impedance of all transmission lines is $Z_0 = 50\Omega$. Ports 2 and 3 are connected to matched power meters.


- (a) Determine the input VSWR and return loss in dB (at port 1).
(b) Determine the insertion loss and isolation of the switch.

[Marks 5,2,2]

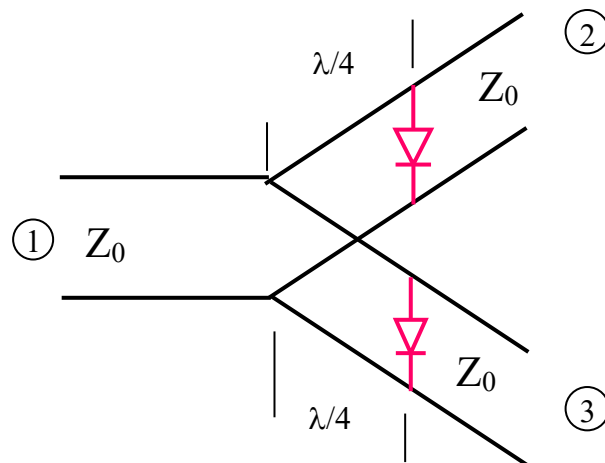

- Q4.** Consider a loaded line phase shifter shown below. Derive expressions for Z_e and θ_e of an equivalent transmission line in terms of normalized susceptance b .

[Marks 8]

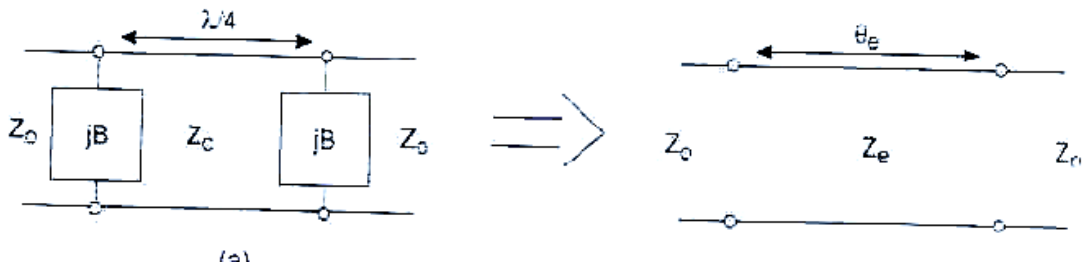

ABCD to S-Parameter Conversion Formulas

$$S_{11} = \frac{1}{\Delta} (A + BY_0 - CZ_0 - D), \quad S_{12} = \frac{2}{\Delta} (AD - BC)$$

$$S_{21} = \frac{2}{\Delta}, \quad S_{22} = \frac{1}{\Delta} (-A + BY_0 - CZ_0 + D)$$

$$\Delta = (A + BY_0 + CZ_0 + D); Y_0 = 1/Z_0$$