

# ELECTRICAL ENGINEERING DEPARTMENT

## EEL202 CIRCUIT THEORY

MAJOR

19/11/2015

13:00-15:00 PM

MM:45

Q1. Solve the following simultaneous differential equations assuming that the system is initially at rest.

$$2x'(t) + 3x(t) + y'(t) + 6y(t) = \delta(t) \quad x'(t) + x(t) + y'(t) + 6y(t) = u(t)$$

In particular, obtain homogenous and particular solutions, the initial conditions at  $t = 0+$  and the values of the constants based on the initial conditions. (6)

Q2. For the network shown in Fig.1, assuming  $L_1 L_2 = M^2$ , obtain expressions for  $I_1(s)$  and  $I_2(s)$ . Also determine expressions for  $i_1(0+)$  and  $i_2(0+)$  using initial value theorem. (6)

Q3. For the network shown in Fig.2, the switch is closed at  $t = 0$ . Determine  $i_1(t)$  and  $i_2(t)$  at  $t = 0-$  and at  $t = 0+$ . Also, determine their derivatives at  $t = 0+$ . (5)

Q4. Determine the  $y$ -parameters of the network shown in Fig.3, assuming that  $\alpha$  is non zero. Express alpha in terms of  $y_{12}$  and  $y_{21}$ . (5)

Q5. Determine if  $Y(s) = \frac{2s^3 + 2s^2 + 3s + 2}{s^2 + 1}$  is PR. If it is PR, then realize it. (5)

Q6. Realize  $Z(s) = \frac{(s+2)(s+4)}{(s+1)(s+5)}$  in Foster-I and Foster-II forms. (5)

Q7. Realize  $Y_{21}(s) = \frac{Ks}{s^3 + 3s^2 + 4s + 2}$  using zeros of transmission method and determine the value of K so realized. (5)

Q8. Realize  $\frac{V_2}{V_1} = \frac{s+2}{s+3}$  using a constant-resistance network. (4)

Q9. Determine if the polynomial  $f(\omega) = \omega^8 - \omega^4 - 2\omega^2 + 2$  is positive for all  $\omega$ . (4)

PTO for figures

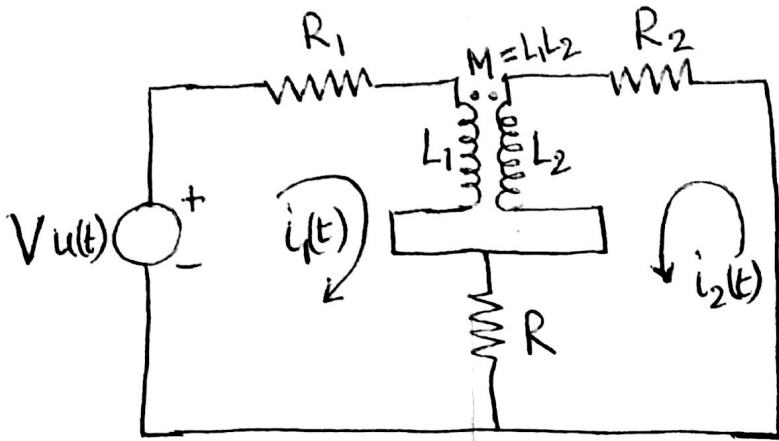


Fig. 1

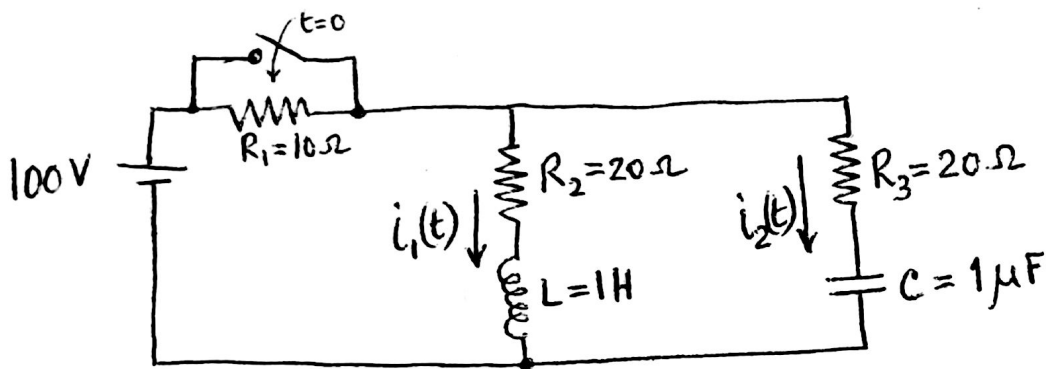


Fig. 2

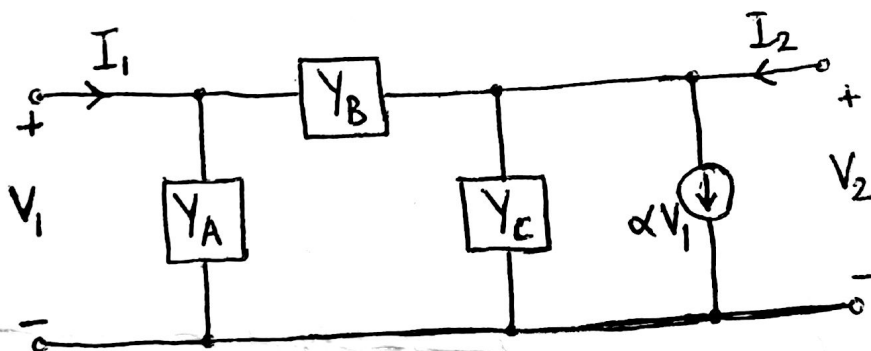


Fig. 3