

# MAJOR EXAMINATION

## POWER ENGINEERING - I (ELL 303)

F.M.: 50


Time: 2 Hours

1. (a) Derive the expression for three phase complex power in terms of sequence components [3]

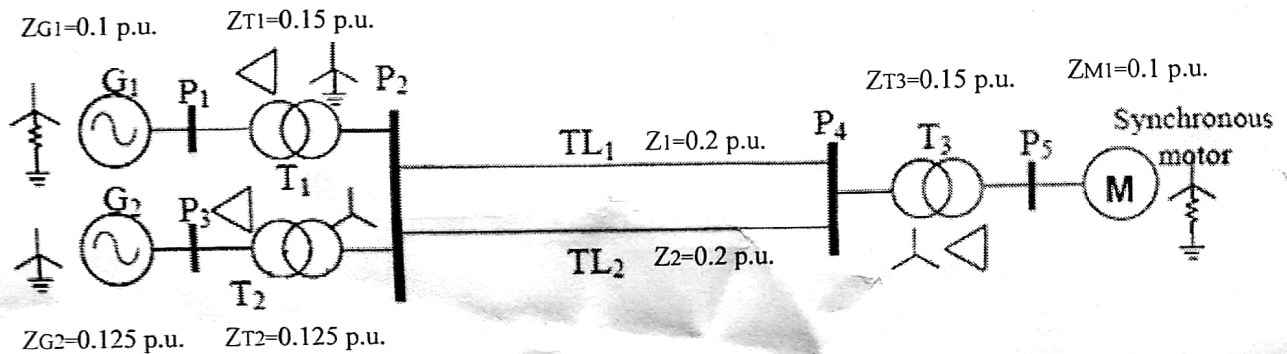(b) Draw the zero sequence network for the figure given below: [5]

(All the values of the p.u. impedances are the zero sequence impedances)

The grounding impedance, wherever present is 0.05 p.u.




2. A three-phase, 50 Hz, 500kV transmission line is 300 km long. The series impedance is  $z=0.045+j0.4 \Omega$  per phase per km and the shunt admittance is  $y=j0.0004 \Omega$  per phase per km. Calculate:

(a) The ABCD parameters of the line. [4]

(b) The transmission line efficiency if receiving end rated load is 800 MW, 0.8 p.f. lag at 500kV. [6]

$P_R = \dots$

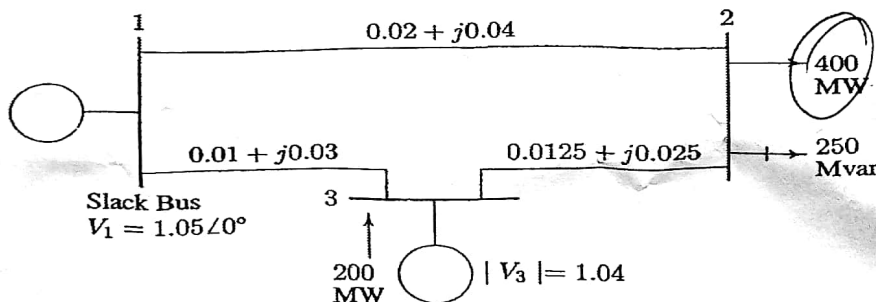3. For the system given below perform one iteration of Newton-Raphson load flow and calculate the line flows. [10]



*Handwritten notes:*  
 PQ  
 V<sub>3</sub>  
 $70 \times 17$   
 $120$

*Handwritten notes:*  
 PV  
 $\delta$


*Handwritten notes:*  
 $3 V_a B_a$   
 $(V_a + V_a' + V_2)(I_a + I_a' + I_2)$

PTO


$p_c = 1$

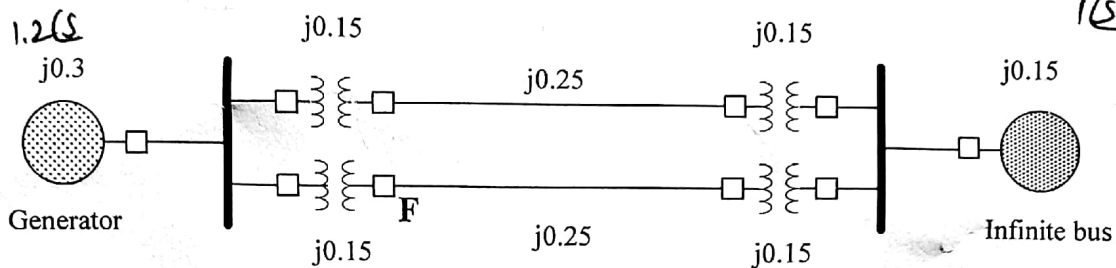4. Determine the critical clearing angle for a generator for a three-phase fault at the point F (in the figure given below) when the generator is delivering 1 p.u power. Assume that the voltage behind transient reactance is 1.2 p.u. for the generator and that the voltage at the infinite bus is 1 p.u. [8]

Show the areas in the P -  $\delta$  diagram. Find the critical clearing angle from the theoretical foundation equating both accelerating and de-accelerating area



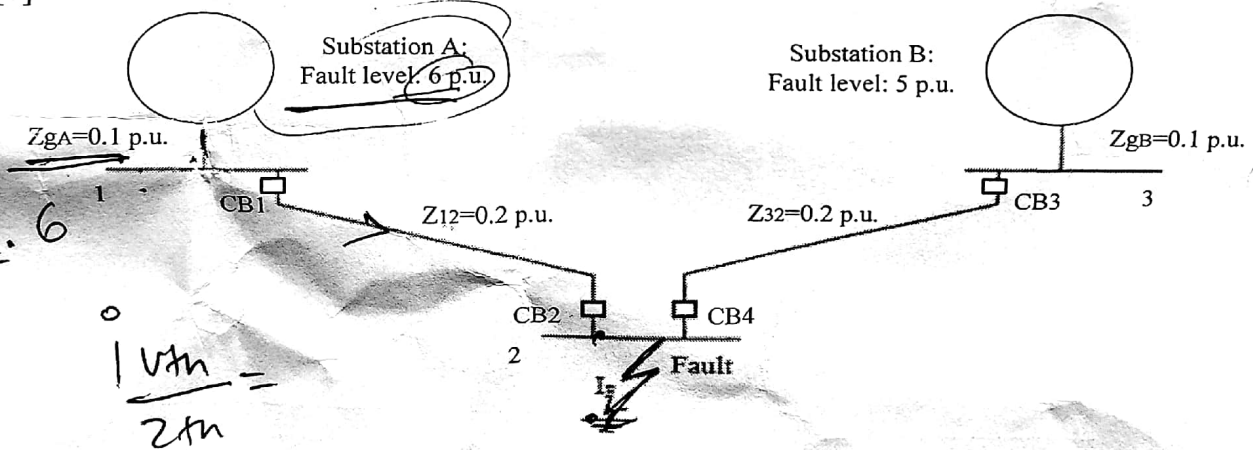5. In the figure given below containing two substations represented by Thevenin equivalent circuit as Substation A and Substation B. The Fault level is the short circuit current level at the substation with a voltage of 1 p.u. Find the fault current following a three-phase dead short circuit at bus number 3. [6]



6. (a) The reactances of an alternator rated 10 MVA, 5 kV are  $X_1 = X_2 = 15\%$  and  $X_0 = 5\%$ . The neutral of the alternator is grounded through a reactance of  $0.4\Omega$ . Single line to ground fault occurs at the terminals of the alternator. Determine the line currents, fault current and the terminal voltages. [4]

- (b) Give a single line diagram of a 132 kV substation with one incoming and two outgoing feeders of 66 kV and 33 kV. Mark all the components used in the substation. [4]

100MM