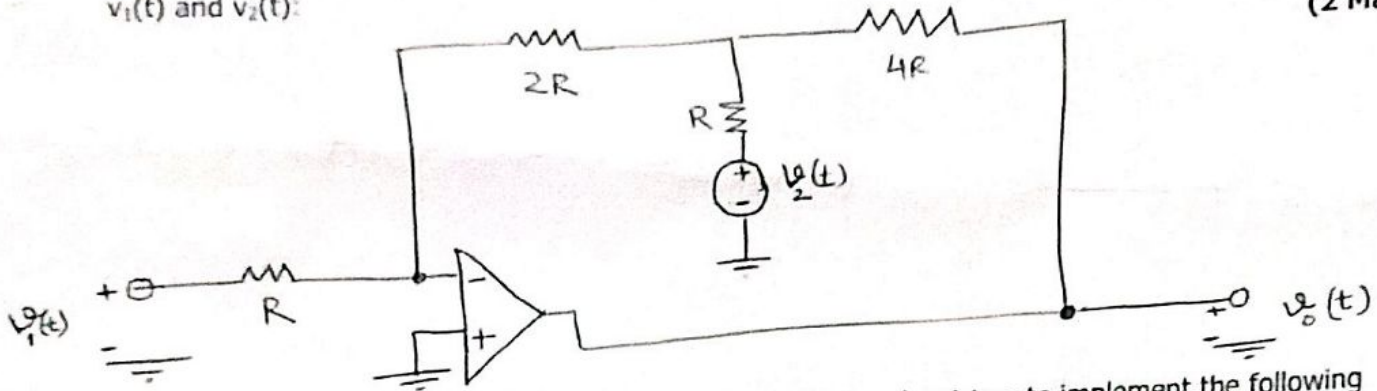


**Q1.** Design a series RLC circuit to select a 100 kHz frequency of a radio. This circuit has a bandwidth of 5 kHz and draws 11 W from a 220 V (rms) source. (3 Marks)

**Q2(a).** For the ideal Op-Amp circuit shown in Figure 1, find the output  $v_o(t)$  as a function of the inputs  $v_1(t)$  and  $v_2(t)$ : (2 Marks)




**Q2(b).** Use Op-Amps, and the correct choice of capacitors and resistors to implement the following function  $y(t)$ , where  $y_1(t)$  is an input signal:

$$y(t) = \frac{d^2 y_1}{dt^2} - 5 \frac{dy_1}{dt}$$

(3 Marks)

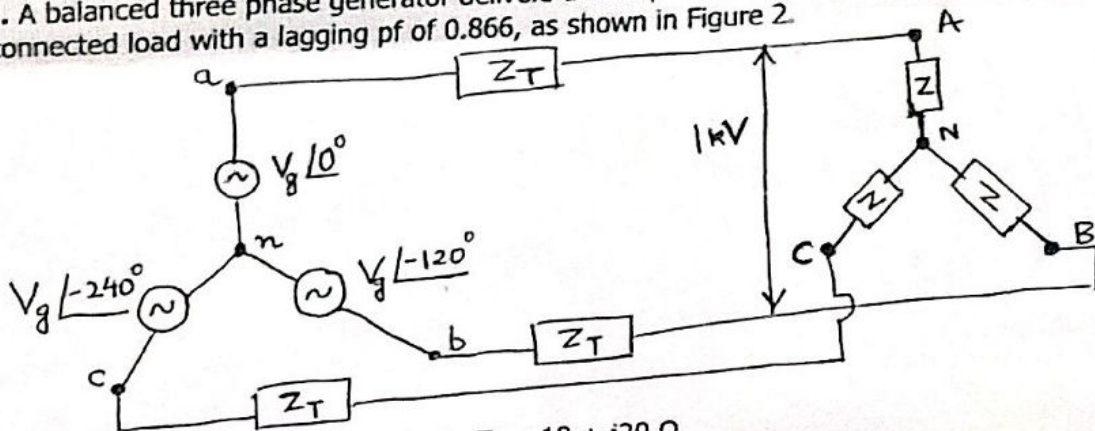**Q3.** A balanced three phase generator delivers a total power of 10 kW at 1 kV to a balanced three phase Y-connected load with a lagging pf of 0.866, as shown in Figure 2.



The transmission line has an impedance  $Z_T = 10 + j20 \Omega$ .

(2 Marks)  
(3 Marks)

- Determine the load impedance  $Z$ .
- Determine the total average power supplied by the generator.

**Q4.** Implement a Digital to Analog Converter (DAC), using Op-Amps and the correct choice of capacitors and/or resistors, for a 4-bit digital input  $v_3 v_2 v_1 v_0$  where  $v_3, v_2, v_1$ , and  $v_0$  are input voltage signals that can have values either '0' V or '1' V. Note a digital signal  $v_3 v_2 v_1 v_0$  has an analog value  $2^0 \times v_0 + 2^1 \times v_1 + 2^2 \times v_2 + 2^3 \times v_3$ . For example, the digital signal 1011 has an analog value  $2^0 \times 1 + 2^1 \times 1 + 2^2 \times 0 + 2^3 \times 1 = 11$ . (3 Marks)

**Q5.** In a power plant, the power is supplied to the plant at 6000V for a 50 Hz operation. The load of the power plant consists of heating (50 kW) and induction motors (200 kVA) that are operating at a lagging power factor of 0.5.

- Calculate the plant power factor (1.5 Marks)
- Calculate the reactive power (1 Marks)
- What reactive load has to be added to correct the power factor of the plant to 0.95? (1.5 Marks)