

**Started on** Wednesday, 19 August 2020, 9:46 AM

**State** Finished

**Completed on** Wednesday, 19 August 2020, 10:56 AM

**Time taken** 1 hour 10 mins

**Grade** 72.00 out of 150.00 (48%)

**Question 1**

Correct

Mark 2.00 out of 2.00

A series RC circuit is fed from single phase AC supply. If the supply frequency is increased, power factor of the circuit will:

Select one:


- A. Increase ✓
- B. Decrease
- C. Remains Same
- D. None of these

**Question 2**

Incorrect

Mark 0.00 out of 2.00

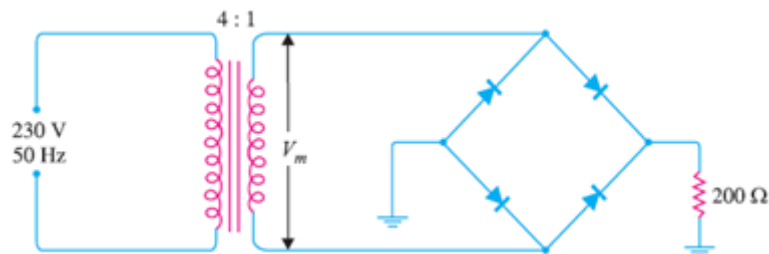In the bridge type circuit shown in Figure, the diodes are assumed to be ideal. Find peak inverse voltage and output frequency. Assume primary to secondary turns to be 4:1 and input AC supply voltage is 230 V (rms), 50 Hz.



Select one:

- A. 91.5 V & 50 Hz
- B. 81.3 V & 100 Hz
- C. 60.2 V & 100 Hz ✗
- D. 75.2 V & 150 Hz

**Question 3**

Correct

Mark 2.00 out of 2.00

The two wattmeter method for 3-phase power measurement is applicable for

Select one:

- A. Only star connected system
- B. Only delta connected system
- C. Both star connected and delta connected system ✓
- D. None of the above

**Question 4**

Incorrect

Mark 0.00 out of 2.00

In a star connected system, the current flowing through the line is

Select one:

- A. Greater than the phase current ✗
- B. Equal to the phase current
- C. Lesser than the phase current
- D. None of these

**Question 5**

Correct

Mark 2.00 out of 2.00

Amplifiers and oscillators using BJT, operate in ..... region

Select one:


- A. Inverted mode
- B. Active ✓
- C. Saturation
- D. Cut-off

**Question 6**

Incorrect

Mark 0.00 out of 2.00

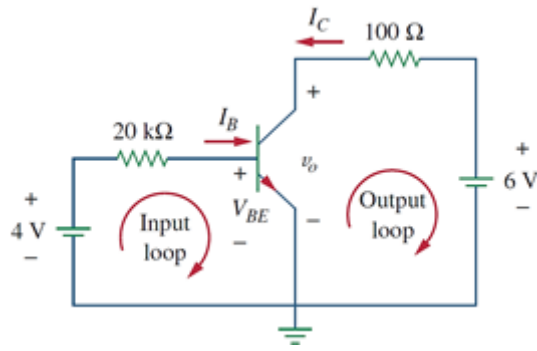Find  $I_B$  in the transistor circuit of given Figure. Assume that the transistor operates in the active mode,  $V_{BE} = 0.7 \text{ V}$  and that  $\beta = 50$ .



Select one:


- A.  $100 \mu\text{A}$
- B.  $135 \mu\text{A}$  ✗
- C.  $165 \mu\text{A}$
- D.  $105 \mu\text{A}$

**Question 7**

Incorrect

Mark 0.00 out of 2.00

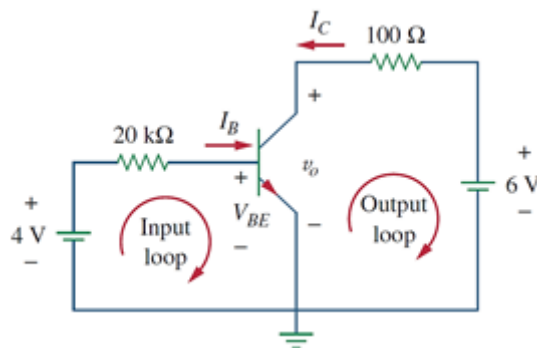Find  $I_C$  in the transistor circuit of given Figure. Assume that the transistor operates in the active mode,  $V_{BE} = 0.7 \text{ V}$  and that  $\beta = 50$ .



Select one:

- A.  $7.75 \text{ mA}$
- B.  $5 \text{ mA}$  ✗
- C.  $10 \text{ mA}$
- D.  $8.25 \text{ mA}$

**Question 8**

Incorrect

Mark 0.00 out of 2.00

A transistor has an  $I_C$  of  $100 \text{ mA}$  and  $I_B$  of  $0.5 \text{ mA}$ . What is the value of  $\alpha_{dc}$ ?

Select one:


- A.  $0.659$
- B.  $0.543$  ✗
- C.  $0.995$
- D.  $0.787$

**Question 9**

Incorrect

Mark 0.00 out of 2.00

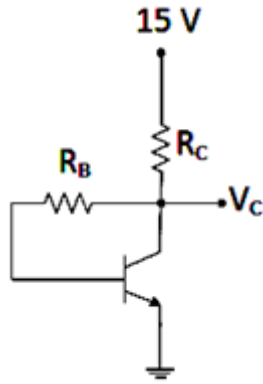In the given circuit, the transistor has  $\beta = 75$ ,  $V_{BE} = 0.7 \text{ V}$  and the collector voltage  $V_c = 9 \text{ V}$ . Then the ratio of  $R_B/R_C$  is



Select one:

- A. 105.13
- B. 99 ✗
- C. 76
- D. 108

**Question 10**

Correct

Mark 2.00 out of 2.00

The power consumed in a circuit element will be least when the phase difference between the current and voltage is

Select one:

- A.  $90^\circ$
- B.  $0^\circ$
- C.  $60^\circ$
- D.  $180^\circ$

**Question 11**

Correct

Mark 2.00 out of 2.00

For the same peak value which of the following wave will have the highest RMS value?

Select one:

- A. Square wave ✓
- B. Half-wave rectified sine wave
- C. Triangular wave
- D. Sine wave

**Question 12**

Correct

Mark 2.00 out of 2.00

The line A to neutral voltage is  $10\angle 15^\circ$  V. For a balanced three phase star-connected load with phase sequence ABC. The voltage of line B with respect to line C is given by

Select one:


- A.  $10\sqrt{3}\angle 105^\circ$  V
- B.  $-10\sqrt{3}\angle 90^\circ$  V
- C.  $10\sqrt{3}\angle -75^\circ$  V
- D.  $10\angle 105^\circ$  V

**Question 13**

Incorrect

Mark 0.00 out of 2.00

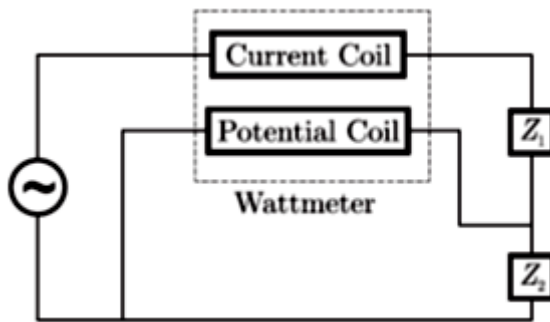A wattmeter is connected as shown in figure. The wattmeter reads.



Select one:

- A. Power consumed by  $Z_2$
- B. Zero always
- C. Total power consumed by  $Z_1$  &  $Z_2$
- D. Power consumed by  $Z_1$  ✗

**Question 14**

Correct

Mark 2.00 out of 2.00

In a series RLC circuit at resonance, the magnitude of the voltage developed across the capacitor

Select one:

- A. can be greater than the input voltage, however, it is  $90^\circ$  out of phase with input voltage ✓
- B. can be greater than the input voltage, and is in phase with input voltage
- C. is always zero
- D. can never be greater than the input voltage

**Question 15**

Incorrect

Mark 0.00 out of 2.00

A two-port device is defined by the following pair of equations:

$$i_1 = 2v_1 + v_2 \text{ and } i_2 = v_1 + v_2; \text{ Its impedance parameters } (z_{11}, z_{12}, z_{21}, z_{22}) \text{ are given by}$$

Select one:


- A. (2,1,1,1) ✗
- B. (1,-1,-1,2)
- C. (1,1,1,2)
- D. (2,-1,-1,1)

**Question 16**

Incorrect

Mark 0.00 out of 2.00

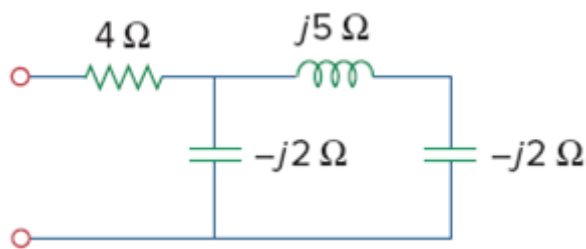Obtain the power factor for the circuit in figure below.



Select one:


- A. pf= 1
- B. pf = 0.8547 (leading) ✗
- C. pf = 0.5547 (leading)
- D. pf = 0.7547 (leading)

**Question 17**

Incorrect

Mark 0.00 out of 2.00

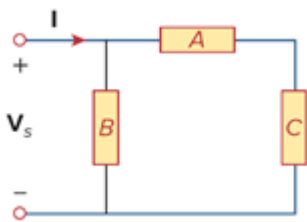In the circuit of the given figure, device A receives 2 kW at 0.8 pf lagging, device B receives 3 kVA at 0.4 pf leading, while device C is inductive and consumes 1 kW and receives 500 VAR. Determine the power factor of the entire system.



Select one:


- A. pf = 0.9845 (leading)
- B. pf = 0.8547 (leading) ✗
- C. pf= 1
- D. pf = 0.7547 (leading)

**Question 18**

Correct

Mark 2.00 out of 2.00

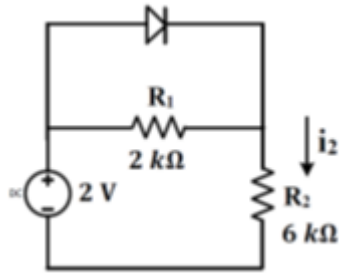Assume that the diode in the figure has  $V_{on} = 0.7 V$ , but is otherwise ideal. The magnitude of the current  $i_2$  (in mA) is equal to \_\_\_\_\_



Select one:


- A. 0.3 mA
- B. 0.216 mA ✓
- C. 0.5 mA
- D. 0.1 mA

**Question 19**

Incorrect

Mark 0.00 out of 2.00

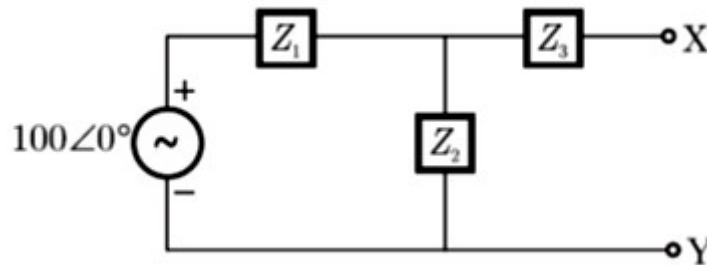In the figure,  $Z_1 = 10 \angle -60^\circ$ ,  $Z_2 = 10 \angle 60^\circ$  and  $Z_3 = 30 + j40$ . Thevenin impedance seen from X-Y is



Select one:


- A.  $\sqrt{35} \angle 75^\circ$
- B.  $\sqrt{60} \angle 30^\circ$
- C.  $\sqrt{70} \angle 30^\circ$
- D.  $\sqrt{56.55} \angle 45^\circ$

**Question 20**

Incorrect

Mark 0.00 out of 2.00

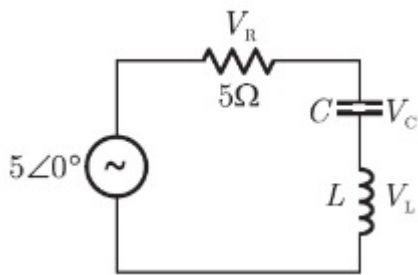In the circuit of given figure, the magnitude of  $V_L$  and  $V_C$  are twice that of  $V_R$ . Given that  $f=50$  Hz , Calculate the inductance of the coil.



Select one:

- A. 1.32 H
- B. 5.3 H ✗
- C. 31.83 mH
- D. 2.14 mH

**Question 21**

Correct

Mark 2.00 out of 2.00

The RMS value of the voltage  $u(t)= 3 + 4 \cos (3t)$  is

Select one:

- A.  $\sqrt{3+2\sqrt{3}}$
- B.  $\sqrt{17}$
- C. 3
- D. 3




**Question 22**

Incorrect

Mark 0.00 out of  
2.00

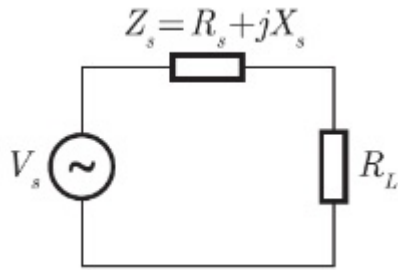A non-ideal voltage source  $V_s$  has an internal impedance of  $Z_s$  (Refer to the circuit below). If a purely resistive load is to be chosen that maximizes the power transferred to the load, its value must be



Select one:


- A. Equal to imaginary part of  $Z_s$
- B. Equal to real part of  $Z_s$  ✗
- C. 0
- D. Equal to magnitude of  $Z_s$

**Question 23**

Correct

Mark 2.00 out of  
2.00

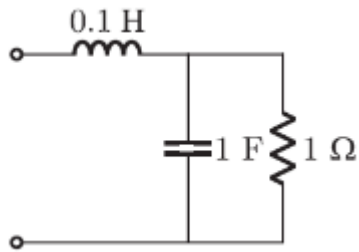Determine the frequency at which the given circuit behaves as a purely resistive circuit.



Select one:


- A. 4 rad/s
- B. 3 rad/s ✓
- C. 2 rad/s
- D. 1 rad/s

**Question 24**

Incorrect

Mark 0.00 out of 2.00

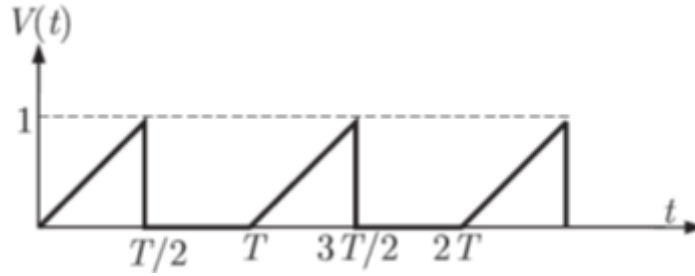For the triangular waveform shown in the figure, the RMS value of the voltage is equal to



Select one:


- A.  $\left(\frac{1}{3}\right)$
- B.  $\left(\sqrt{\frac{1}{3}}\right)$
- C.  $\left(\sqrt{\frac{1}{6}}\right)$
- D.  $\left(\sqrt{\frac{2}{3}}\right)$

**Question 25**

Incorrect

Mark 0.00 out of 2.00

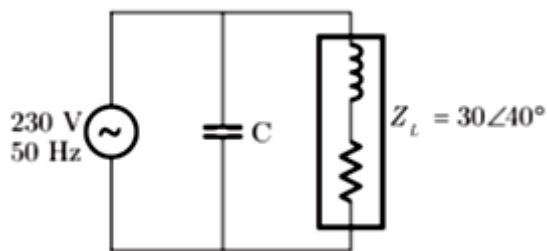In the circuit shown in Figure, what value of  $C$  will cause a unity power factor at the ac source?



Select one:


- A.  $6.81 \mu\text{F}$
- B.  $165 \mu\text{F}$
- C.  $0.681 \mu\text{F}$
- D.  $68.2 \mu\text{F}$

**Question 26**

Correct

Mark 4.00 out of 4.00

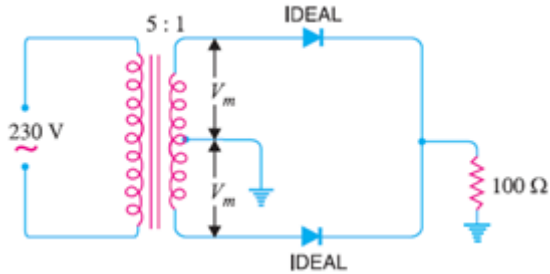In the centre-tap circuit shown in Figure, the diodes are assumed to be ideal i.e. having zero internal resistance. Find peak inverse voltage (*in volts*). Assume that input AC supply voltage is 230 V (rms).




Answer: 65.05

**Question 27**

Incorrect

Mark 0.00 out of 4.00

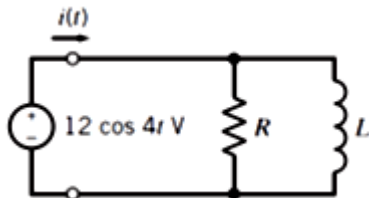The complex power delivered by the voltage source shown in the figure below is  $S = 18 + j9$  VA. Determine the value of inductance  $L$  (*in henrys*).




Answer: 4

**Question 28**

Correct

Mark 4.00 out of 4.00

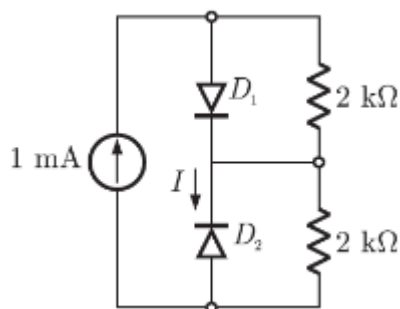Assume that  $D_1$  and  $D_2$  in figure are ideal diodes. The value of current  $I$  (*in mA*) through  $D_2$  is



Answer: 0



**Question 29**

Correct

Mark 4.00 out of 4.00

In a series R–L circuit the voltage magnitude across the resistance R is 12V and the voltage magnitude across the inductance L is 5V. Find the supply voltage magnitude (*in volts*).

Answer:  ✓**Question 30**

Correct

Mark 4.00 out of 4.00


The average power delivered (*in watts*) to an impedance  $(4 - j3) \Omega$  by a current  $5 \cos(100\pi t + 100) \text{ A}$  is

Answer:  ✓**Question 31**

Incorrect

Mark 0.00 out of 4.00

Find the  $Y_{22}$  (*in siemens*) parameters for the two port network of given figure.

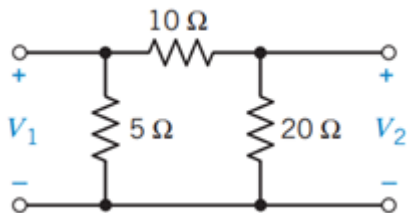Answer:  ✗**Question 32**

Correct

Mark 4.00 out of 4.00

When port 1 of a two-port circuit is short-circuited,  $I_1 = 4I_2$  and  $V_2 = 0.25I_2$ . Find the value of admittance parameter  $Y_{12}$  (*in siemens*).

Answer:  ✓**Question 33**

Correct

Mark 4.00 out of 4.00

In a series RLC circuit,  $R = 10 \Omega$ ,  $X_L = 20 \Omega$ ,  $X_C = 20 \Omega$  and supply voltage peak value  $V_m = 100 \text{ V}$ . What is the peak value of voltage (*in volts*) across the capacitor?

Answer:  ✓

**Question 34**

Correct

Mark 4.00 out of 4.00

A 240-V rms 60-Hz supply serves a load that is 10 kW (resistive), 15 kVAR (capacitive), and 22 kVAR (inductive). Find the apparent power of the load in kVA.

Answer:  ✓

**Question 35**

Correct

Mark 4.00 out of 4.00

In a series RLC circuit, the rms voltage across elements at resonant frequency are  $V_C = 125$  V,  $V_L = 125$  V, and  $V_R = 40$  V. What is the value of source voltage rms magnitude (in volts)?

Answer:  ✓

**Question 36**

Correct

Mark 4.00 out of 4.00

What is the upper half power frequency (in Hz) for a series RLC circuit that resonates at 2000 Hz and has a bandwidth of 200 Hz?


Answer:  ✓

**Question 37**

Correct

Mark 4.00 out of 4.00

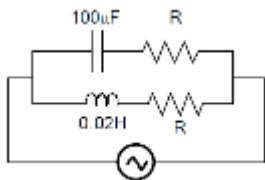The circuit below is excited by a sinusoidal source. Determine value of R, in  $\Omega$ , for which the admittance of the circuit becomes a pure conductance at all frequencies.




Answer:  ✓

**Question 38**

Incorrect

Mark 0.00 out of 4.00

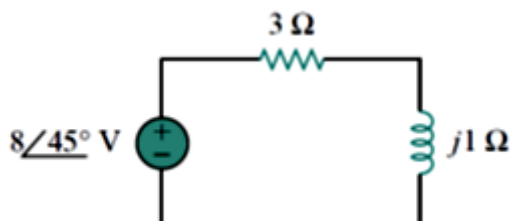For the circuit shown in figure, calculate the total reactive power, in VAR, of the circuit if the supply voltage rms value is  $8 \angle 45^\circ$  V.



Answer:  ✗

**Question 39**

Correct

Mark 4.00 out of 4.00


Calculate the average power absorbed (in watts) by the passive linear network if  $v(t) = 80 \cos(10t + 20^\circ) \text{ V}$ , and  $i(t) = 15 \sin(10t + 60^\circ) \text{ A}$ .

Answer:  ✓**Question 40**

Incorrect

Mark 0.00 out of 4.00


For the circuit shown in figure  $D_1$  and  $D_2$  are ideal diodes. Determine the current  $i_{D2}$  (in mA).

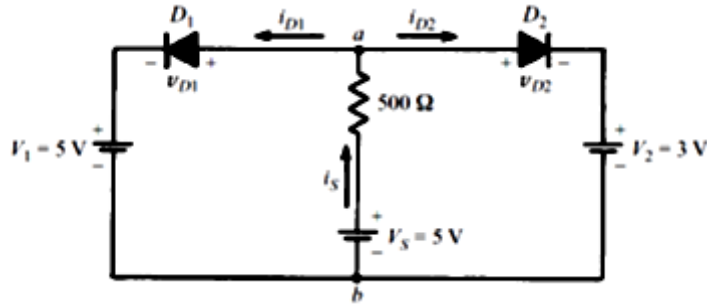Answer:  ✗**Question 41**

Correct

Mark 4.00 out of 4.00


The circuit of the given figure adds a dc level (a bias voltage) to a signal whose average value is zero. If  $v_S$  is a 10-V square wave (oscillating between +10 V and -10 V) of period  $T$ ,  $R_L = R_1 = 10 \Omega$ , and the diode is ideal, find the average value of  $v_L$  (in volts).

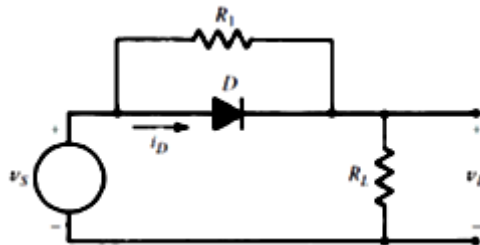Answer:  ✓**Question 42**

Correct

Mark 4.00 out of 4.00

Find the rms value of the full-wave rectified sine wave in Figure.

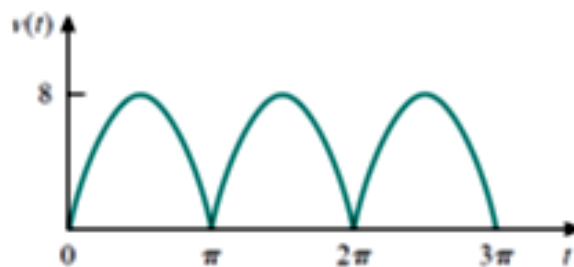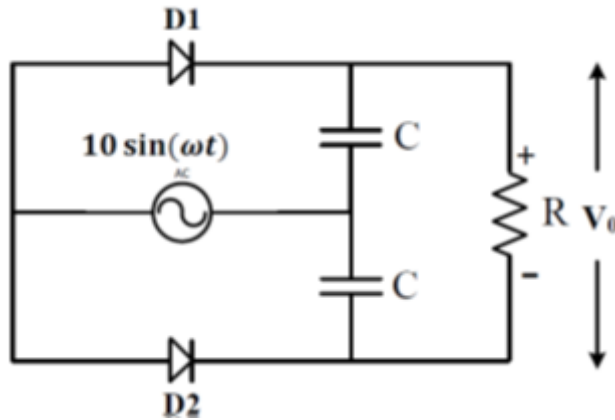
Answer:  ✓

**Question 43**

Incorrect

Mark 0.00 out of 4.00


The diodes D1 and D2 in the figure are ideal and the capacitors are identical. The product  $RC$  is very large compared to the time period of the AC voltage. Assuming that the diodes do not breakdown in the reverse bias, the output voltage  $V_0$  (in volt) at the steady-state is  ❌

**Question 44**

Incorrect

Mark 0.00 out of 4.00

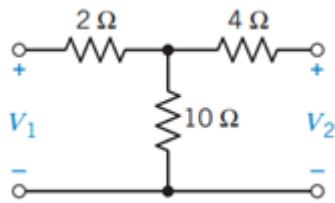Find the transmission parameter  $D$  of the circuit shown below.




Answer:  ❌

**Question 45**

Incorrect

Mark 0.00 out of 4.00

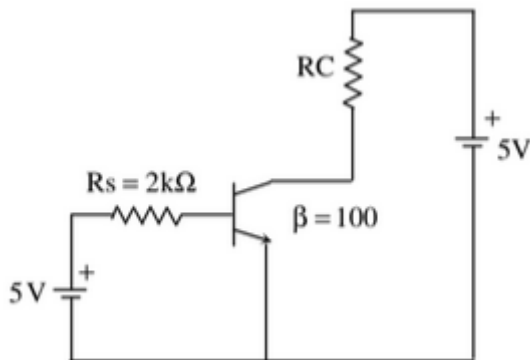The transistor in the given circuit should always be in active region. Take  $V_{CE(sat)} = 0.2V$ ;  $V_{BE} = 0.7V$ . The maximum value of  $R_C$  in  $\Omega$  which can be used is



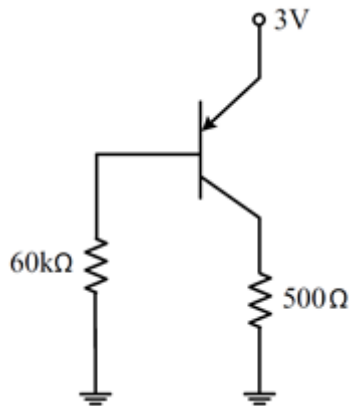
Answer:  ❌

**Question 46**

Incorrect

Mark 0.00 out of 4.00

In the circuit shown in the figure, the BJT has a current gain ( $\beta$ ) of 50. For an emitter – base voltage  $V_{EB} = 600 \text{ mV}$ , the emitter – collector voltage  $V_{EC}$  (in volts) is

 ✘
**Question 47**

Incorrect

Mark 0.00 out of 4.00

A three-phase motor can be regarded as a balanced Y-load. A three-phase motor draws 5.6 kW when the line voltage is 220 V and the line current is 18.2 A. Determine the power factor of the motor.


Answer:  ✘

**Question 48**

Incorrect

Mark 0.00 out of 4.00

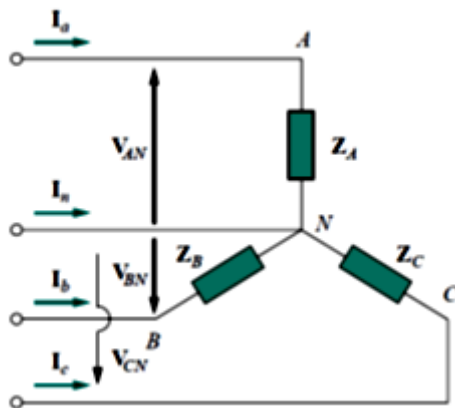The unbalanced Y-load of shown Figure has balanced voltages of 100 V and the *acb* sequence. Calculate the magnitude of neutral current  $I_n$  (in Amperes). Take ( $Z_A = 15 \, \Omega$ ,  $Z_B = 10 + j5 \, \Omega$ ,  $Z_C = 6 - j8 \, \Omega$ .)



Answer:  ✘



**Question 49**

Incorrect

Mark 0.00 out of  
4.00

The two-wattmeter method produces wattmeter readings  $W_1 = 1560$  W and  $W_2 = 2100$  W, when connected to a balanced delta-connected load. If the rms line voltage is 220 V, calculate the per phase reactive power (*in VAR*) of the load.

Answer:  ❌**Question 50**

Incorrect

Mark 0.00 out of  
4.00

A balanced Y-connected load with a phase impedance of  $(8 + j6)$   $\Omega$  is connected to a balanced three-phase source with a rms line voltage of 220 V. Calculate the magnitude of the line current  $I_L$  (*in Amperes*).

Answer:  ❌

◀ Mock Test ELL100 (15 th Aug 2020)



LAB QUIZ-II (22 - Aug - 2020) ▶