

**Started on** Wednesday, 30 December 2020, 10:00 AM

**State** Finished

**Completed on** Wednesday, 30 December 2020, 12:55 PM

**Time taken** 2 hours 55 mins

**Marks** 23.00/40.00

**Grade** 5.75 out of 10.00 (58%)

**Question 1**

Correct

Mark 1.50 out of  
1.50

A coil consists of 1000 turns of copper wire having a cross-sectional area of 1 millimeter-square. The mean length per turn is 40 *cm* and the resistivity of copper is  $0.02 \mu\Omega\text{-m}$ .

The resistance (in ohms) of the coil

✓

One possible correct answer is: 8


The power absorbed (in Watts) by the coil when connected across 120 Volts D.C. supply

✓

One possible correct answer is: 1800

**Question 2**

Correct

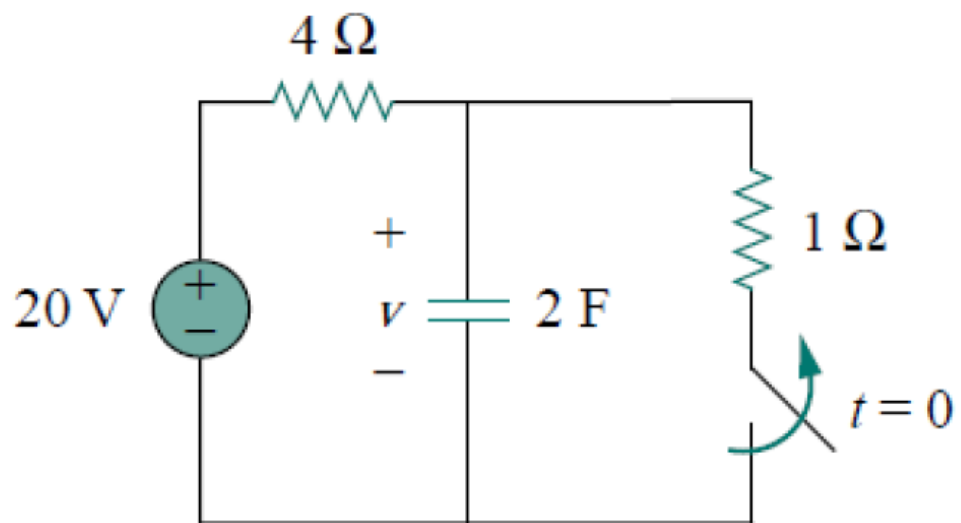Mark 2.00 out of  
2.00The capacitor's voltage for  $t < 0$  is ✓

One possible correct answer is: 4

Capacitor's voltage at  $t = 3$  seconds is ✓

One possible correct answer is: 9.003

Your answer is correct.

**Question 3**

Partially correct

Mark 0.50 out of  
2.00

Three loads are connected in parallel to a 120 Vrms source with zero degrees phase. Load 1 absorbs 60 kVAR at  $\text{pf} = 0.85$

lagging, load 2 absorbs 90 kW and 50 kVAR leading, and load 3 absorbs 100 kW at  $\text{pf} = 1$ .

Equivalent impedance is (insert the real part in the first box and the imaginary part in the second box)

❌

One possible correct answer is: 0.05, 0.0017

Power factor of the parallel combination is

✅

One possible correct answer is: 0.9994

Current supplied by the source is (insert the magnitude in the first box and the phase in the second box)

❌

One possible correct answer is: 2.391, -0.083

Your answer is partially correct.

You have correctly answered 1 part(s) of this question.

**Question 4**

Partially correct

Mark 1.00 out of  
2.00

Find the complex power when

 $P = 169\text{W}$  and  $Q = 150\text{VAR}$  (insert the real part in the first box and the imaginary part in the second box)

One possible correct answer is: 269, -150

 $Q = 2000\text{V}$  and  $\text{pf} = 0.9$  (lagging) (insert the real part in the first box and the imaginary part in the second box)

One possible correct answer is: 4129

 $S = 600\text{VA}$  and  $Q = 450\text{VAR}$  (inductive) (insert the real part in the first box and the imaginary part in the second box)

One possible correct answer is: 396.9, 450

 $V_{\text{rms}} = 220\text{V}$ ,  $P = 1\text{kW}$ ,  $|Z| = 40\ \Omega$  (Inductive) (insert the real part in the first box and the imaginary part in the second box)

One possible correct answer is: 1000, 681.2

Your answer is partially correct.

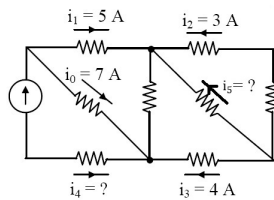
You have correctly answered 2 part(s) of this question.

**Question 5**

Correct

Mark 1.00 out of  
1.00

In the circuit given below:

What is the value of current  $i_4$  (in Ampere)

One possible correct answer is: -12

What is the value of current  $i_5$  (in Ampere)


One possible correct answer is: -7

Your answer is correct.

**Question 6**

Partially correct

Mark 1.00 out of 4.00

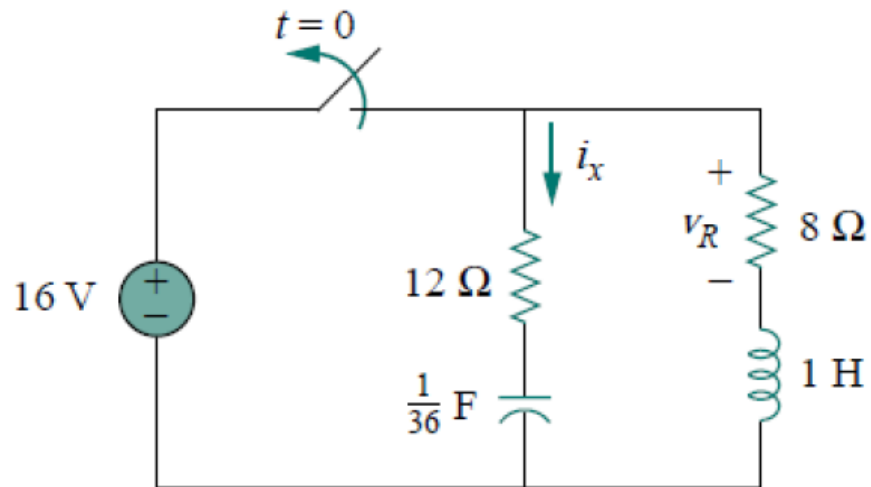

Sum of the roots of the characteristic equation is

 ✓

One possible correct answer is: -20

 $i_x$  at  $t = 3$  seconds is ✗

One possible correct answer is: -0.00185

 $v_R$  at  $t = 5$  seconds is ✗

One possible correct answer is: 0.000272


Your answer is partially correct.

You have correctly answered 1 part(s) of this question.

### Question 7

Incorrect

Mark 0.00 out of  
2.00

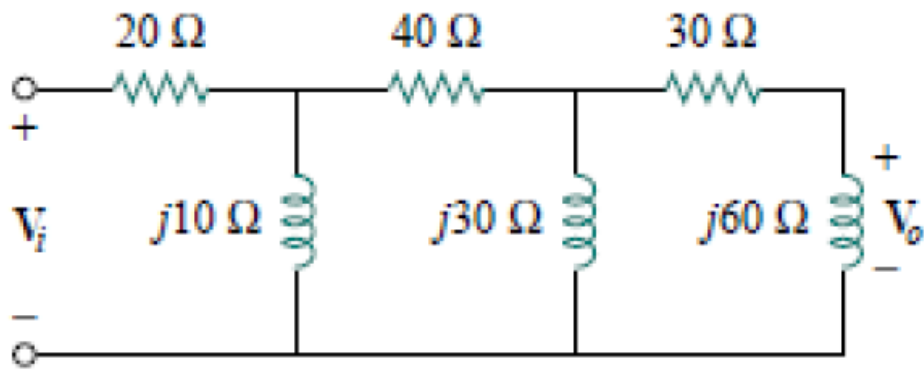

The phase shift of  $V_o$  with respect to  $V_i$  is

✘

One possible correct answer is: 140.2

The magnitude of the output  $V_o$  when input is 120V

✘

One possible correct answer is: 18.43

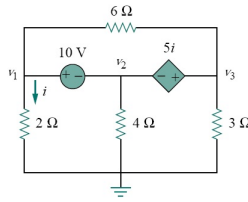
Your answer is incorrect.

**Question 8**

Correct

Mark 3.00 out of  
3.00

Apply the nodal analysis in the circuit shown below:

Find  $v_1$  (in Volts) in the circuit ✓

One possible correct answer is: 3.04

Find  $v_2$  (in Volts) in the circuit ✓

One possible correct answer is: -6.96

Find  $v_3$  (in Volts) in the circuit ✓

One possible correct answer is: 0.65

Your answer is correct.




**Question 9**

Correct

Mark 2.00 out of  
2.00

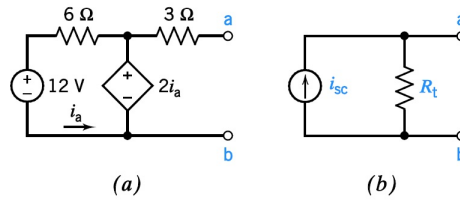Determine values of  $R_t$  (in Ohms) and  $i_{sc}$  (in Amperes) that cause the circuit shown in Fig. b to be the Norton equivalent circuit of the circuit in Fig. a.



The value of  $i_{sc}$  (in Amperes)

 ✓

One possible correct answer is: -2

The value of  $R_t$  (in Ohms)


 ✓

One possible correct answer is: 3

Your answer is correct.

**Question 10**

Incorrect

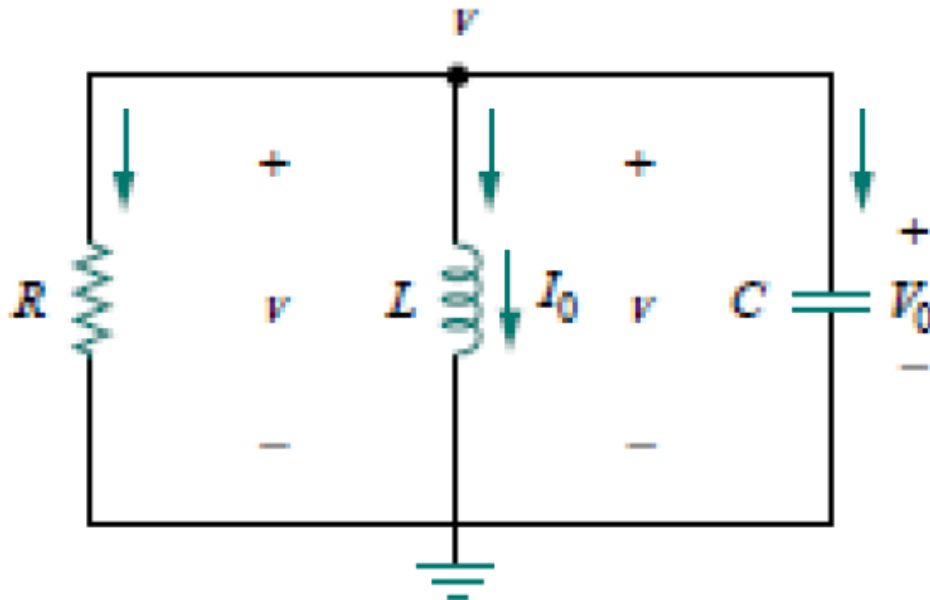Mark 0.00 out of  
2.00

With  $R = 2$  Ohms,  $L = 0.4$ H and  $C = 25$ mF,  $v_0(0) = 0$ ,  $i_0(0) = 3$ A, then  $v(t)$  at  $t = 0.1$  seconds is

 ✘

One possible correct answer is: -4.41455

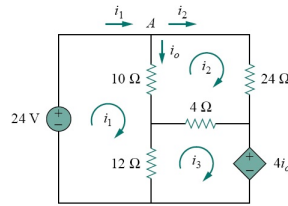
Your answer is incorrect.

**Question 11**

Incorrect

Mark 0.00 out of  
2.00

Use mesh analysis in the circuit shown below:

Find the current  $i_1$  (in Amperes) ✘

One possible correct answer is: 2.25

Find the current  $i_2$  (in Amperes) ✘

One possible correct answer is: 0.75

Find the current  $i_3$  (in Amperes) ✘

One possible correct answer is: 1.5

Find the current  $i_0$  (in Amperes) ✘

One possible correct answer is: 1.5

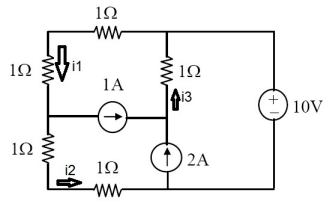
Your answer is incorrect.

**Question 12**

Partially correct

Mark 0.50 out of  
2.00

Consider the circuit below:

Find the value of  $i_1$  (in Ampere) ✘

One possible correct answer is: 3

Find the value of  $i_2$  (in Ampere) ✘

One possible correct answer is: 2

Find the value of  $i_3$  (in Ampere) ✔

One possible correct answer is: 3

Power supplied by the voltage source (in Watts)

 ✘

One possible correct answer is: 0


Your answer is partially correct.

You have correctly answered 1 part(s) of this question.

**Question 13**

Incorrect

Mark 0.00 out of 2.00

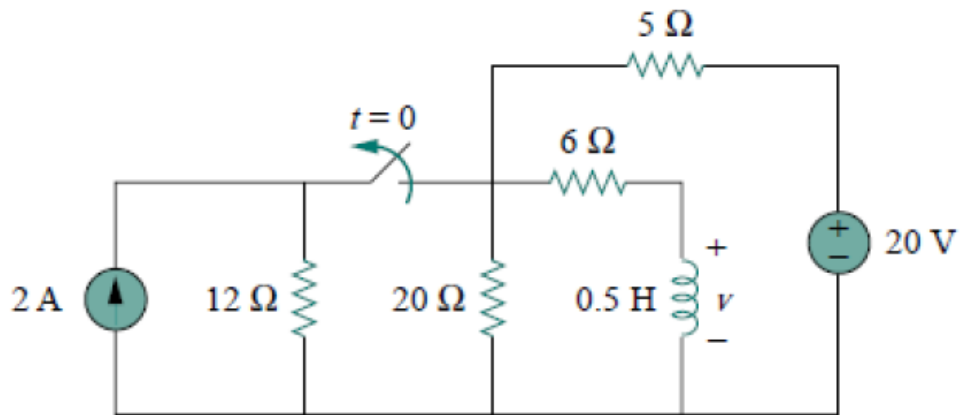

$v(t)$  at  $t = 0.04$  seconds is

 ✘


One possible correct answer is: -1.7973

Your answer is incorrect.

**Question 14**

Correct

Mark 2.00 out of 2.00

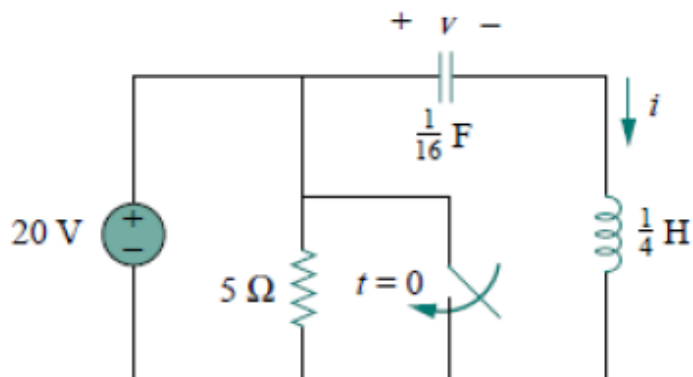

Value of  $i(t)$  at  $t = \pi/24$  seconds is


 ✔

One possible correct answer is: -8.66

Your answer is correct.

**Question 15**

Partially correct

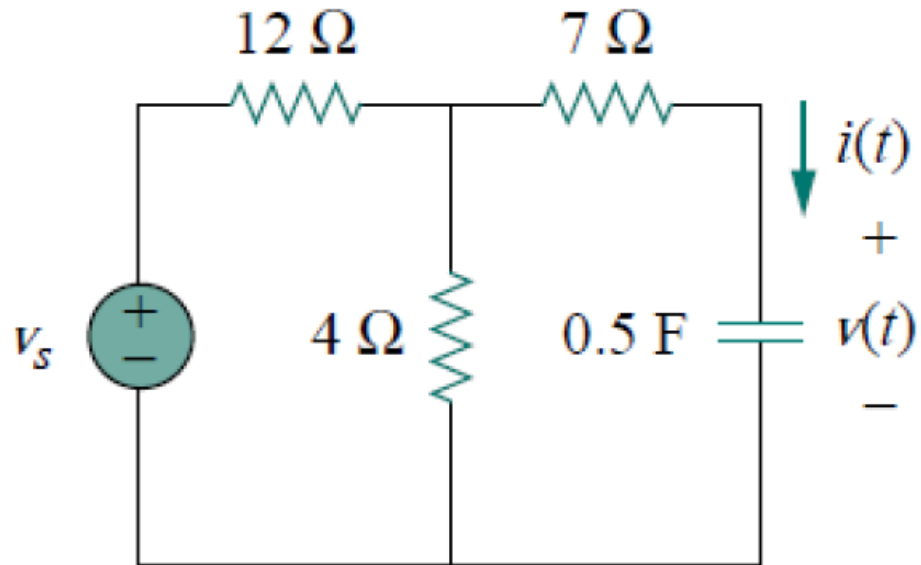Mark 1.00 out of  
2.00

The input  $V_s = 5 u(t)$ , where  $u(t)$  is the step function. The step response  $v(t)$  at  $t = 10$  seconds is

 ✓

One possible correct answer is: 1.08083

The input  $V_s = 5 u(t)$ , where  $u(t)$  is the step function. Step response  $i(t)$  at  $t = 5$  seconds is

 ✗

One possible correct answer is: 0.0459

Your answer is partially correct.


You have correctly answered 1 part(s) of this question.

**Question 16**

Correct

Mark 2.00 out of 2.00

Consider the circuit shown below

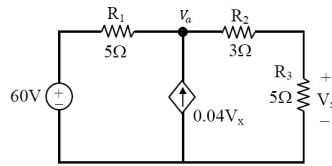

The absolute value of current flowing through resistance R1 in Ampere

 ✓

One possible correct answer is: 4

The absolute value of current flowing through resistance R2 in Ampere

 ✓

One possible correct answer is: 5

The value of the node voltage Va in Volts

 ✓

One possible correct answer is: 40



Your answer is correct.

**Question 17**

Correct

Mark 1.50 out of 1.50

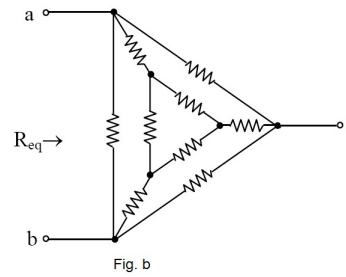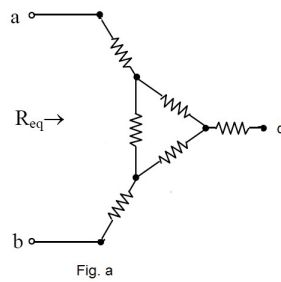Consider the circuits shown in Fig. a and Fig. b below, where each resistor has a value equal to  $1 \Omega$ :



The equivalent resistance (in Ohms) across the terminals a and b in Fig. a is?

 ✓

One possible correct answer is: 2.67

The equivalent resistance (in Ohms) across the terminals a and b in Fig. b is?

 ✓

One possible correct answer is: 0.53

Your answer is correct.




**Question 18**

Correct

Mark 2.00 out of  
2.00

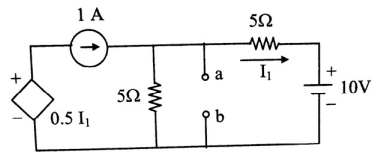For the circuit shown below, Thevenin's voltage and Thevenin's resistance between terminals a and b are:



Select one:

- 4 Volts and 2 Ohm
- 5 Volts and 2 Ohm
- 7.5 Volts and 2.5 Ohms ✓
- 3 Volts and 2.5 Ohms

Your answer is correct.

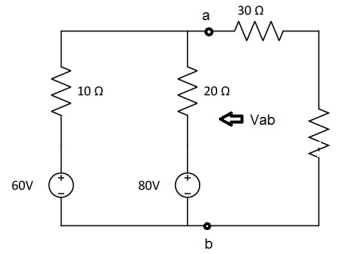
The correct answer is: 7.5 Volts and 2.5 Ohms

**Question 19**

Partially correct

Mark 2.00 out of 3.00

Consider the circuit shown below, where R is the load resistance:

Find the open circuit voltage between terminals a and b, i.e.,  $V_{ab}$  in volts ✓

One possible correct answer is: 66.67

Find the value of load resistance R (in ohms) for maximum power transfer

 ✓

One possible correct answer is: 36.67

Find the value of maximum power transferred to the load R in watts

 ✗

One possible correct answer is: 60.61

Your answer is partially correct.

You have correctly answered 2 part(s) of this question.

[◀ Solutions to Tutorial 5](#)

Lecture 19 (Digital Electronics) ▶