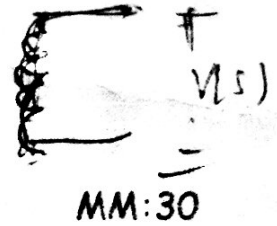


# ELECTRICAL ENGINEERING DEPARTMENT

## ELL202 CIRCUIT THEORY



MINOR II

07/10/2016

09:30-10:30

MM:30

Q1. The switch S in the network shown in Fig.1 is opened at  $t=0$ . Starting with the transformed network, determine the voltage across the switch for  $t>0$ . (8)

Q2. The switch in the network shown in Fig.2 is in position *a* until a steady state is reached. At  $t=0$ , the switch is moved to position *b*. Determine the transform of the voltage across the capacitor using Thevenin's theorem. (6)

Q3. Two poles of the double-tuned circuit shown in Fig.3 are located at  $s=-4+j70$  and at  $s=-4+j80$ . Determine the values of all network elements assuming that  $R=1$  ohm. What will be the shape of the magnitude response of the voltage transfer function for this network? Determine all possible information about the magnitude response. (8)

Q4. Determine the h-parameters of the network in Fig.4 from the basic definition of these parameters. Draw the transform domain diagrams for computation of each parameter. (8)

