

Minor-II: ELL302

Time: 60 minutes

Max. Marks: 25

Note: (i) Draw neat waveforms to scale (if needed)

1. Waveforms of a 3-phase rectifier feeding an R-L load ($R=0.1 \Omega$, $L=1.0 \text{ H}$) are shown in Fig. 1. Identify the waveforms with proper justification. (7)
2. A single-phase full-wave controlled bridge rectifier is feeding an inductive load (I_0). Through mathematical analysis determine the (a) magnitude of the predominant harmonic present in the ac source current waveform (8)
(b) the per unit value of seventh harmonic.
(Assume rms value of input source current as base value)
3. A 48 to 12 V, 18 W, 100 kHz step-down converter (feeding a 12 V battery load) inductor current waveform shown in Fig. 2. Determine the switching frequency of the device, if the load on converter is reduced to 6 W a switch duty ratio of 40%. Assume switch and diode conducts for equal durations. (10)


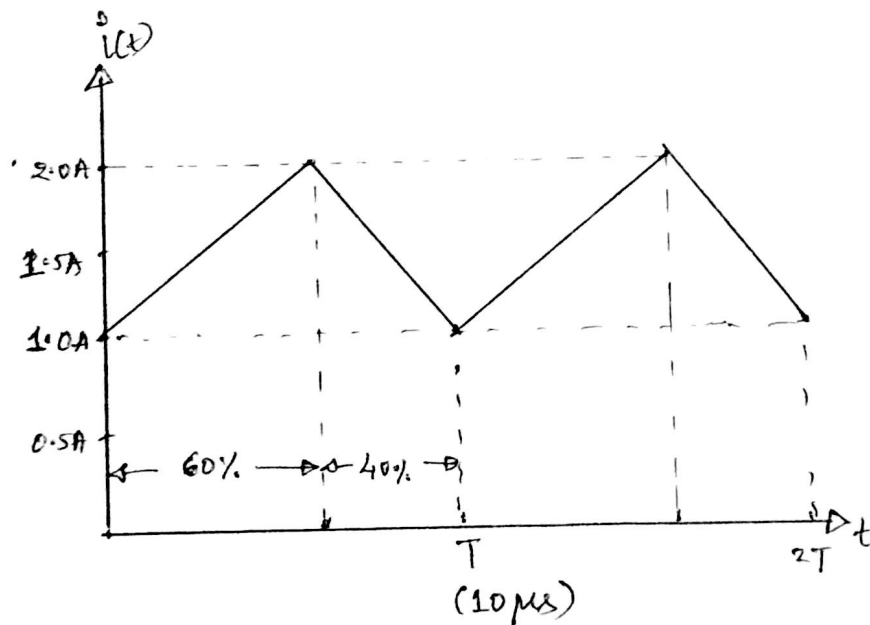



Fig. 2

Fig. 1


X1

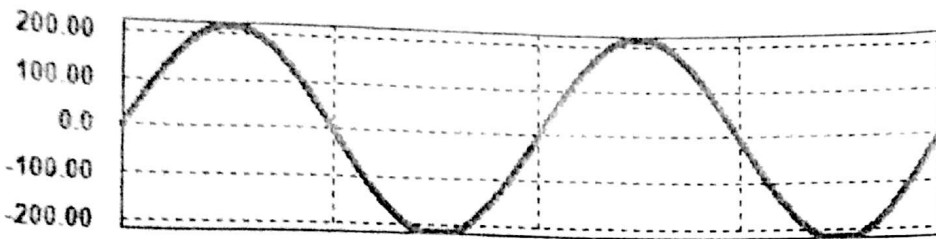


X2

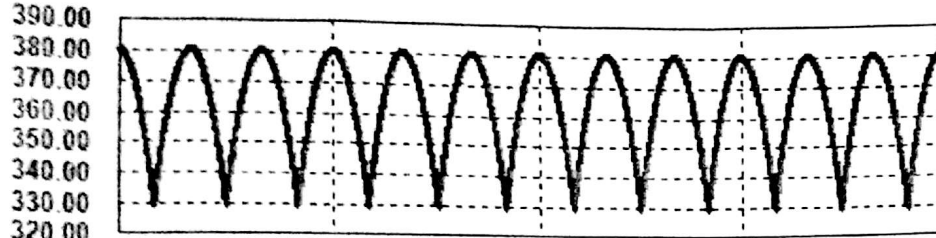


X3

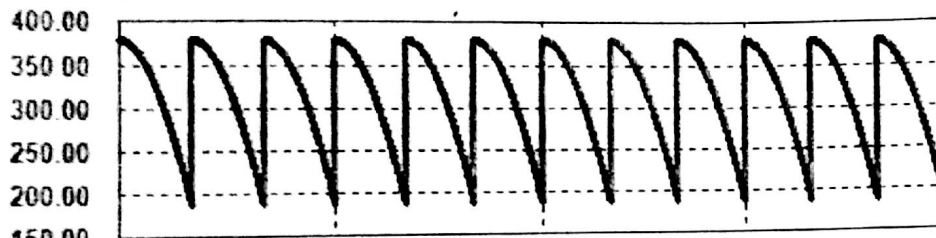


X4

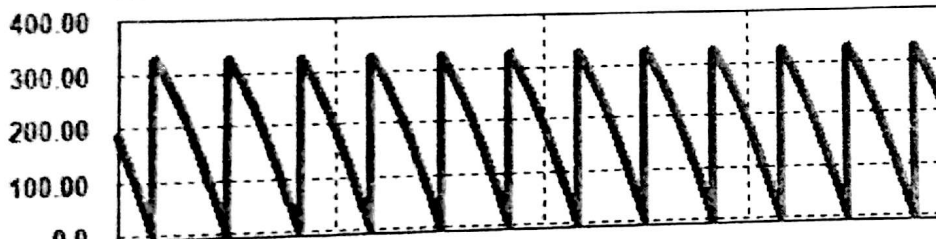

X5

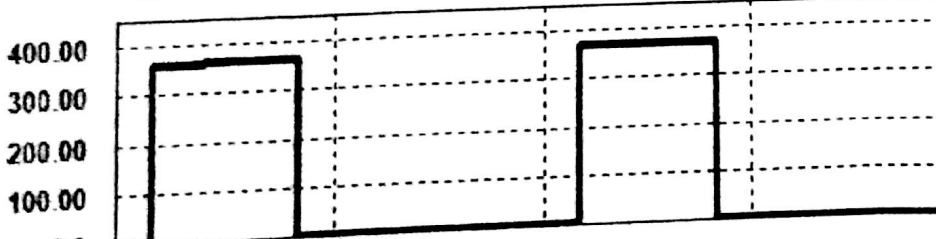

X6

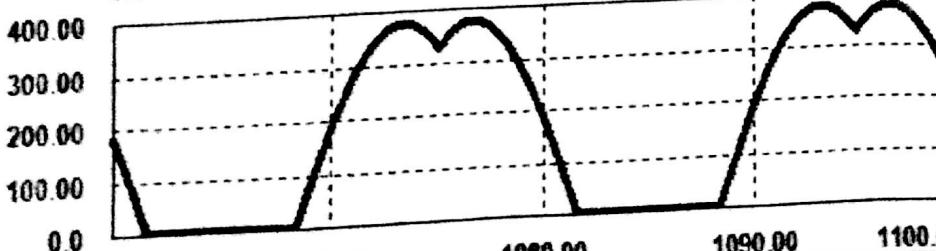

X1: V_{source}
 $V_{phase} = V_m \sin(\omega t)$
 $V_m = 220V$ (1)

X2:
 $V = \sqrt{3} V_m \sin(\omega t + \frac{\pi}{6})$
 $V_m = 220V$ (1)
 3-phase, 6-pulse rectifier
 $\omega t \in (2\pi n - \frac{\pi}{6}, 2\pi n + \frac{\pi}{6})$

X3:
 2230° (1)

X4:
 2260° (1)

X5:
 Current waveform
 0.5

X6:
 3-phase, half wave
 rectifier (0)
 Devices conducting sequence:
 61, 12, 23, 34, 45, 56