


MAJOR EXAMINATION

POWER ENGINEERING - I (ELL 303)


F.M.: 50

Time: 2 Hours

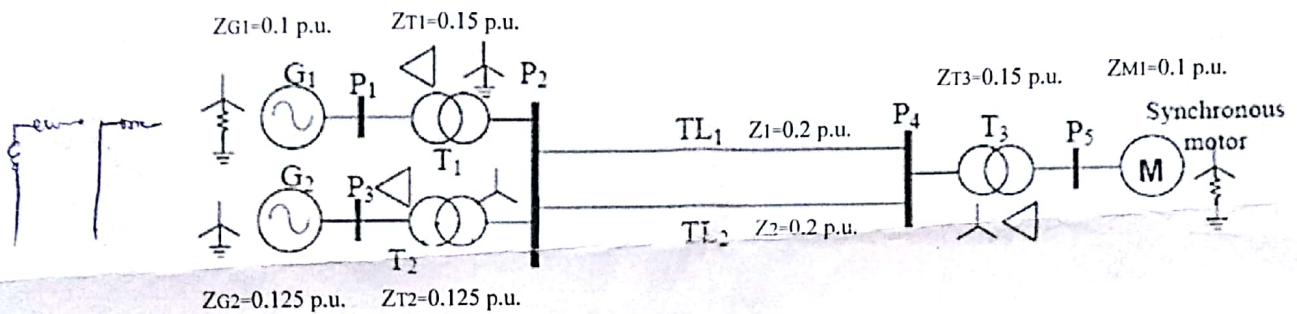1. (a) Derive the expression for three phase complex power in terms of sequence components [3]
 (b) Draw the zero sequence network for the figure given below: [5]
 (All the values of the p.u. impedances are the zero sequence impedances)
 The grounding impedance, wherever present is 0.05 p.u.



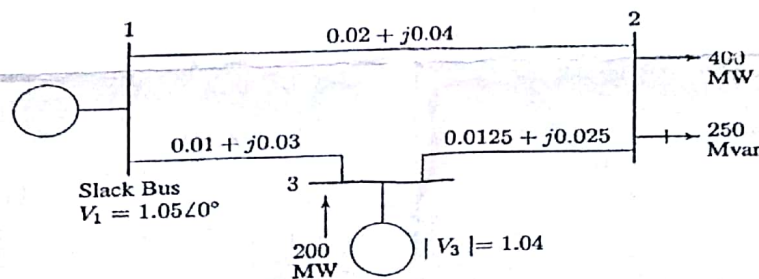2. A three-phase, 50 Hz, 500kV transmission line is 300 km long. The series impedance is $z = 0.045 + j0.4 \Omega$ per phase per km and the shunt admittance is $y = j0.0004 \Omega$ per phase per km. Calculate:
 (a) The ABCD parameters of the line. [4]
 (b) The transmission line efficiency if receiving end rated load is 800 MW, 0.8 p.f. lag at 500kV. [6]
3. For the system given below perform one iteration of Newton-Raphson load flow and calculate the line flows. [10]




PTO

P_2
 P_3
 \textcircled{Q}
 $0.0325 + j0.065$
 $V_2 I_2^* =$
 $\frac{83.58}{86.82}$
 170.4

$$\frac{e^{xL} + e^{-xL}}{2} = \cosh xL$$


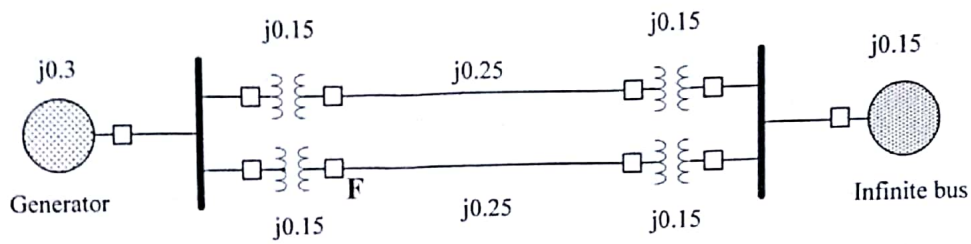
4. Determine the critical clearing angle for a generator for a three-phase fault at the point F (in the figure given below) when the generator is delivering 1 p.u power. Assume that the voltage behind transient reactance is 1.2 p.u. for the generator and that the voltage at the infinite bus is 1 p.u. [8]

Show the areas in the P - δ diagram. Find the critical clearing angle from the theoretical foundation equating both accelerating and de-accelerating area



$$\frac{0.3}{0.55} = \frac{0.3}{2}$$

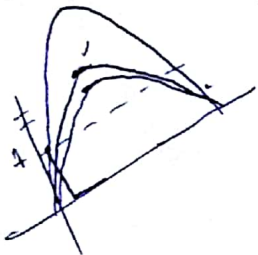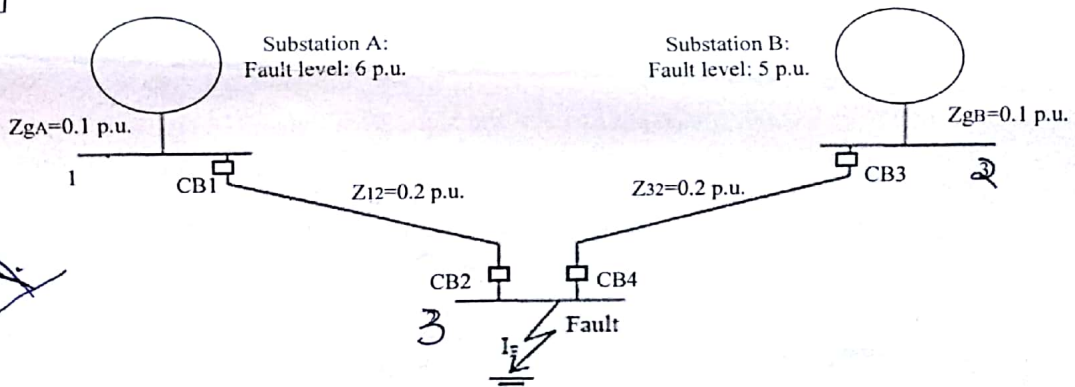5. In the figure given below containing two substations represented by Thevenin equivalent circuit as Substation A and Substation B. The Fault level is the short circuit current level at the substation with a voltage of 1 p.u.. Find the fault current following a three-phase dead short circuit at bus number 3. [6]



6. (a) The reactances of an alternator rated 10 MVA, 5 kV are $X_1 = X_2 = 15\%$ and $X_0 = 5\%$. The neutral of the alternator is grounded through a reactance of 0.4Ω . Single line to ground fault occurs at the terminals of the alternator. Determine the line currents, fault current and the terminal voltages. [4]

- (b) Give a single line diagram of a 132 kV substation with one incoming and two outgoing feeders of 66 kV and 33 kV. Mark all the components used in the substation. [4]

13125

ALL THE BEST

$$\frac{25}{10}$$

$$Z = 0.25$$

$$0.7$$

$$0.7$$

$$2.5 \times \frac{15}{100}$$