

MINOR – II Examination

ELL – 303 (Power Engineering - I)

Time : 1 Hour

Full Marks : 20

- 1(a) Prove that although the equivalent impedance of a transformer referred to either LV side or HV side are different, the pu value of impedance is independent of LV or HV side. [2]
- (b) What are the assumptions considered for Decoupled load flow? [1]
- (c) Why do we perform short circuit studies? [1]
- (d) A 100 MVA, 13.8 kV, Y-connected, 3 phase 50 Hz synchronous generator is operating at the rated voltage and no load when a 3 phase fault occurs at its terminals. Its reactances in per unit to the machine's own base are  $x'' = 0.125$  pu,  $x' = 0.25$  pu and  $x_s = 0.5$  pu. Find the subtransient, transient and steady state fault current in ampere. [1.5]
- (e) Why the subtransient, transient and steady state reactances of an alternator are different? [1]

2. A linearized system showing relation between mismatches and corrections for a 30 bus system is given as :

$$\begin{bmatrix} \Delta P \\ \Delta Q \end{bmatrix} = \begin{bmatrix} J_{11} & J_{12} \\ J_{21} & J_{22} \end{bmatrix} \begin{bmatrix} \Delta \delta \\ \Delta V \end{bmatrix}$$

Where notations have usual meanings. Bus 1 is a slack bus. Bus no. 2 to 10 are PV buses and bus no. 11 to 30 are PQ buses.

- (a) Write down size of each of the submatrix for this system. [2]
- (b) If bus no. 10 is made PQ bus rather than a PV bus, indicate which of the above submatrices will experience change in their size (only indicate the submatrices/vectors). [2]

3. The bus admittance matrix of a 3-bus system is given as: [4]

$$Y_{bus} = \begin{bmatrix} 20 - j50 & -10 + j20 & -10 + j30 \\ -10 + j20 & 26 - j52 & -16 + j32 \\ -10 + j30 & -16 + j32 & 26 - j62 \end{bmatrix}$$

Bus 1: Slack Bus  
 $|V_1|^{spc} = 1.05$  p.u.  
 $\delta_1^{spc} = 0$

Bus 2: PQ bus  
 $P_2^{spc} = -4$  p.u.  
 $Q_2^{spc} = -2.5$  p.u.

Bus 3: PV bus  
 $|V_3|^{spc} = 1.04$  p.u.  
 $P_3^{spc} = 2$  p.u.

Output for 5<sup>th</sup> iteration is  $\delta_2 = -0.047665$   $\delta_3 = -0.008713$   $|V_3|^{spc} = 0.973116$  p.u.

Calculate the output for the 6<sup>th</sup> iteration using FDLF.

4. An electric power system is shown in Figure below with the parameters as specified below. [4+1.5]

G1 : 90 MVA 20 kV, X = 9%    T1 : 80 MVA 20/200 kV, X = 16%  
 G2 : 90 MVA 18 kV, X = 9%    T2 : 80 MVA 200/20 kV, X = 20%  
 Line: 200 kV X = 120 ohms    Load: 200 kV S = 48 MW +j 64 Mvar

Draw the impedance diagram in pu (Assume base MVA as 100 and 20 kV as the voltage base for generator)  
 If there is a three-phase fault at the middle of the line find the fault current (just before fault the voltage at the middle of the line is 190 kV)

