

8

Indian Institute of Technology, Delhi Department of Electrical Engineering

Exam: Major Exam
Course: ELL769 (ELECTRICAL SYSTEMS FOR CONSTRUCTION INDUSTRIES)
Date/Time: Wednesday, 06th April 2022, 14.15 pm – 16.15 pm
Mode: Offline, LHC-619, Closed book exam.
Max Marks: 50 Marks
Note: Make suitable assumptions, wherever necessary.

1. Find the angle by which i_1 lags v_1 if $v_1 = 120 \cos(120\pi t - 40^\circ)$ V and i_1 equals $(-0.8 \cos(120\pi t - 110^\circ))$ A. (Marks 2)
2. The voltage $8 \text{ Ang}(-50^\circ)$ V at a frequency $\omega = 100$ rad/s is applied to a 4 H inductor, and determine the phasor current and the time-domain current. (Marks 3)
3. A $100 \mu\text{F}$ capacitor and an 5 mH inductor, excited at $\omega = 10,000$ rad/s, are connected in parallel. Find the equivalent impedance. (Marks 2)
4. In the frequency-domain circuit of Fig. 1., find (a) I_1 ; (b) I_2 ; (c) I_3 in polar form. (Marks 6)

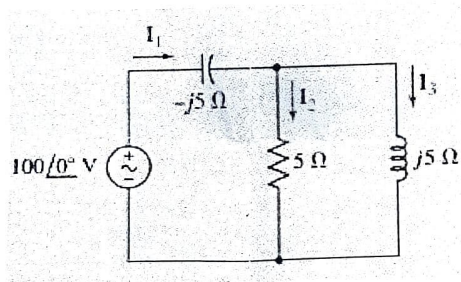


Fig.1.

5. A voltage $V = 115\sqrt{2} \text{ Ang}(45^\circ)$ V is applied across an impedance $Z = 16.26 \text{ Ang}(19.3^\circ)$. Obtain an expression for the instantaneous power, and compute the average power, if $\omega = 50$ rad/s (Marks 4)
6. Calculate the effective value of (a) $6 \cos 25t + 5 \cos 2(25t)$ and (b) $6 \cos 25t + 5 \sin 30t + 4$. (Marks 4)
7. Calculate the average power delivered to the impedance $6 \text{ Ang}(25^\circ)$ Ohm by the current $I = 2 + j5$ A. (Marks 2)
8. A particular circuit is composed of the series combination of a sinusoidal voltage source $3 \cos(100t - 3^\circ)$ V, a 500 Ohm resistor, a 30 mH inductor, and an unknown impedance. If we are assured that the voltage source is delivering maximum average power to the unknown impedance, what is its value? (Marks 2)
9. A balanced three-phase system with a line voltage of 300 V is supplying a balanced Y-connected load with 1200 W at a leading PF of 0.8. Find the line current and the per-phase load impedance. (Marks 3)
10. Solve the above question for a Delta connected load. (Marks 3)

11. For the circuit of Fig. 2., determine the power factor of the combined loads if $Z_L = 10 \text{ Ohm}$.

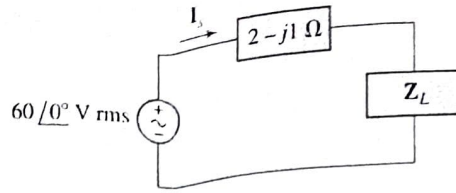


Fig.2.

(Marks 3)

12. A speaker of $9 \text{ } \Omega$, resistive impedance is connected to a supply of 10 V with internal resistive impedance of $1 \text{ } \Omega$, as shown in Fig. 3(a).

(a) Determine the power absorbed by the speaker.

(b) To maximize the power transfer to the speaker, an ideal transformer of $1 : 3$ turns ratio is used between source and speaker as shown in Fig. 3(b). Determine the power taken by the speaker.

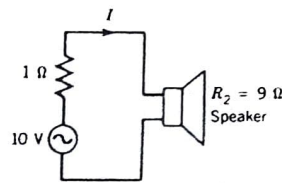


Fig. 3(a)

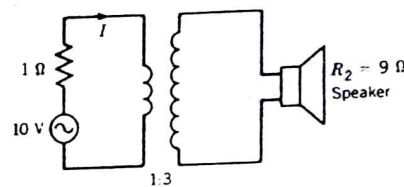


Fig. 3(b)

13. Tests are performed on a 1ϕ , 10 kVA , $2200/220 \text{ V}$, 60 Hz transformer and the following results are obtained

| | Open-Circuit Test (high-voltage side open) | Short-Circuit Test (low-voltage side shorted) |
|-----------|---|--|
| Voltmeter | 220 V | 150 V |
| Ammeter | 2.5 A | 4.55 A |
| Wattmeter | 100 W | 215 W |

Derive the parameters for the approximate equivalent circuits referred to the low-voltage side.

14. Determine v_x in the circuit of Fig. 4.

(Marks 2)

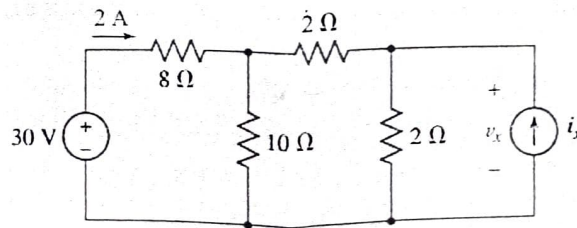


Fig. 4.

15. Determine v in the circuit of Fig. 5.

(Marks 2)

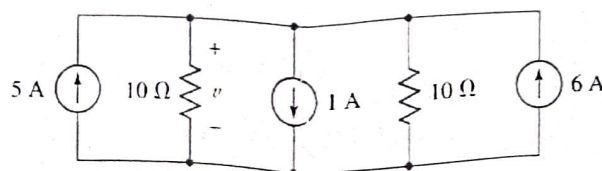


Fig. 5.