


28 Aug 2016

711 Minor-1

Max 20 marks Max 1 hour


Attempt all questions. Make neat diagrams. Be brief, to the point.

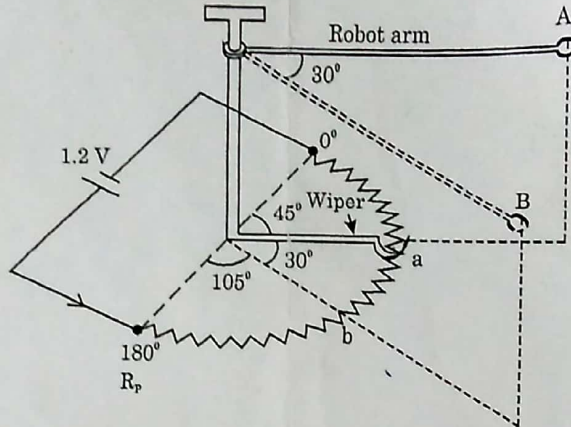Q1 The angular motion of a robotic arm is to be measured by a semi-circular potentiometer as shown in the diagram. The robotic arm moves from the initial position A to the final position B, and corresponding the potentiometer wiper moves from location a to b as shown in the diagram covering an angle of 30° . The total possible wiper movement is 180 degrees. The wiper when at a is having an angle of 45° as shown in the diagram. The potentiometer with $R_p = 1000$ ohms is excited by 1.2 V battery with polarity as shown. It is desired that an offset and sensitivity circuit is added to the system such that the output (at OPAMP output) is 0 V when the arm is at A, and 5 V when the arm is at B. Draw the OPAMP circuit and give its design. Make suitable assumptions where required



- Draw the complete Circuit for above requirement. (3)
- Derive formula for gain of the OP AMP circuit (3)
- Draw, explain working, and Justify the choice of OFF SET circuit (2)
- Explain working of SENSITIVITY set circuit, what precautions be taken. (2)
- Explain a method of calibrating linear displacement sensor with any one standard (4)

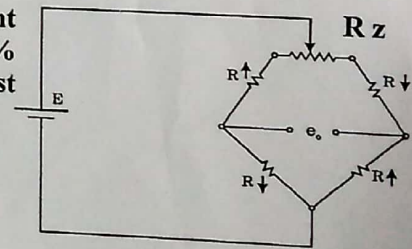Q.2a A strain gauge bridge circuit as shown has a zero adjustment potentiometer R_z . If the tolerance of strain gauge resistance R is $\pm 10\%$, derive the smallest value of R_z (in terms of R), which can zero adjust the bridge in the worst tolerance case (3 marks)



Q.2b A strain gauge bridge circuit as shown has a sensitivity adjustment potentiometer R_s as shown. If the gauge factor G due to manufacturing tolerances can have highest value G_{max} and lowest value G_{min} . Derive minimum value of R_s (in terms of R) that can adjust the sensitivity as G varies between its extreme values. (3 marks)

